

WORKSHEET 8A Q4 WORKED EXAMPLE

Work Sheet 8 A. Series and Parallel problems - Words.

For each problem DRAW the circuit, put the information from the question onto the drawing and then solve using - guess who's law.

1. Three resistors are connected in parallel and then this combination is connected in series with a 10 Ohm resistor. When 500 Volts is applied to the circuit, 25 Amps flows in the 10 Ohm series resistor. If 2 of the parallel resistors are 28 Ohms each then what is the value of the unknown resistor, and what is the current through it and the voltage drop across it ?
2. A heating element is in two sections, each of 45 Ohms. Find the current drawn from the supply (230V) when the sections are connected in a) series and b) parallel ?
3. Two cables having resistances of 0.5 Ohms and 0.8 Ohms carry between them a current of 30 Amps. What is the current in each cable and the Voltage Drop that occurs when the current is flowing ?
4. A cable carries a current of 45 Amps and when that happens a voltage drop of 21 Volts occurs. What would be the resistance value of a cable connected in parallel with the first to reduce the voltage drop to 5% of 230 Volts.
5. The specification for a wire to be used in a wire wound resistor says that its resistance is 0.6 Ohms per meter. How many meters would be required to give :
 - a) A resistance of 3.7 Ohms, and
 - b) 0.2 Ohms, given that the wire must be at least a meter long to reach from one end of the resistor to the other ?
6. A circuit consists of three resistors initially connected in series and then in parallel. What in general terms occurs to the following, given the changes listed.

Series

Parallel

Supply current:
if Voltage is doubled ?


Total resistance:
if one resistor is removed ?

Supply voltage :
if the current has halved ?

Total current:
if an extra resistor is added ?

Voltage drop across each resistor:
if an extra resistor is added ?

Current situation:

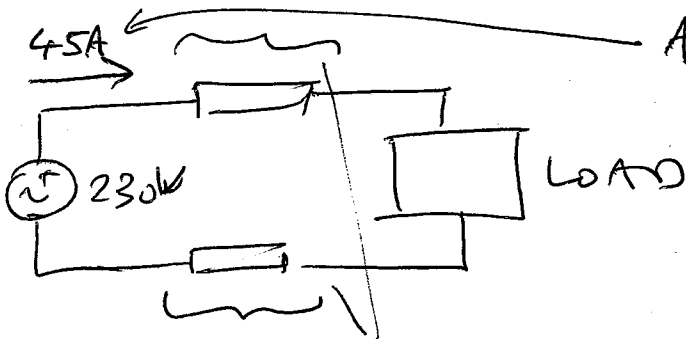

Assume that load current is not affected by volt drop.

Total cable resistance (R_c) causes 21 volts drop at 45A.

We need to reduce this volt drop to 50%.

The target volt drop: $50\% \cdot 230 = 11.5V$
 current volt drop: $= 21V$

Current cable resistance: $\frac{21}{45} = 0.4667 \Omega$

Target cable resistance: $\frac{11.5}{45} = 0.2556 \Omega$

We need to find a resistance to place in parallel with 0.4667Ω to make it look like 0.2556Ω .

Use parallel resistance formula:



$$\frac{1}{0.2556} = \frac{1}{0.4667} + \frac{1}{R_x}$$

$$3.913 = 2.143 + \frac{1}{R_c}$$

$$\frac{1}{R_c} = 1.770$$

$$R_c = 0.5649 \Omega$$

Cross-check.

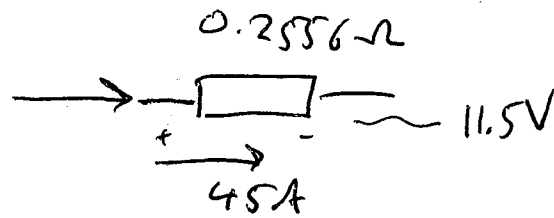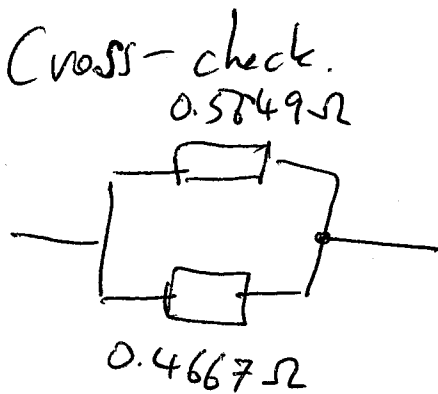

volt drop:

$$0.2556 \cdot 45 = 11.5V$$

which is 5% of 230V.

The parallel cable must have a resistance of 0.5849Ω or below.