



WeiTec

Te Whare Wānanga o te Awakairangi

A

DC fundamentals EE3103

Student workbook 2020 for Ohms and Kirchhoffs laws with Series and parallel exercises



Student name

**WORKSHEET ASSIGNMENT ON RESISTOR CIRCUIT
WORKSHEETS**

WORKSHEET CHECKLIST


	WORKSHEET NUMBER	TICK FINISHED
<u>OHMS LAW</u>		
BASIC	1A	
	1B	
	1C	
SERIES	2A	
	2B	
	3A	
PARALLEL	5A	
	6A	
<u>RESISTIVE NETWORKS</u>		
	10A	
	10B	
	10C	
	10D	
	11A	
	11B	
<u>SERIES-PARALLEL</u>		
	15A	
	15B	
	8A	
	16A	
	16C	
LESSON ON BATTERY INTERNAL RESISTANCE		
INTERNAL R	9A	
<u>HARD SERIES-PARALLEL</u>		
	16D	
	16E	
2 Assignment questions	assignment	
Tutor sign off for workbook completion		signature

$$I = \frac{V}{R}$$


Applies to either a **whole circuit** or a **part of a circuit** and all three factors must **all** apply to the same components

OHMS LAW

SERIES RESISTIVE

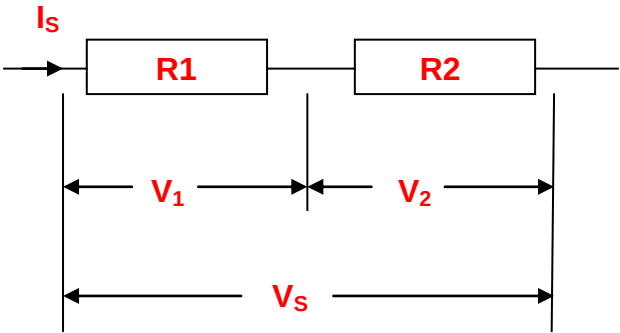


PARALLEL RESISTIVE

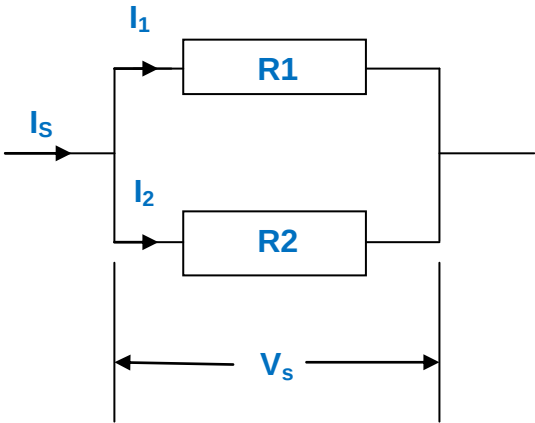


CURRENT CONSTANT		$I_s = I_1 + I_2$ <i>Kirchhoffs current law</i>
$V_s = V_1 + V_2$ <i>Kirchhoffs voltage law</i>		VOLTAGE CONSTANT
$R_T = R_1 + R_2$		$R_T^{-1} = R_1^{-1} + R_2^{-1}$

Ohms Law. Work Sheet 1A Basic calculations.


Fill out this triangle now

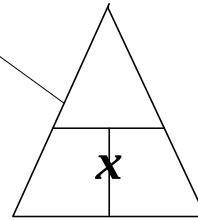

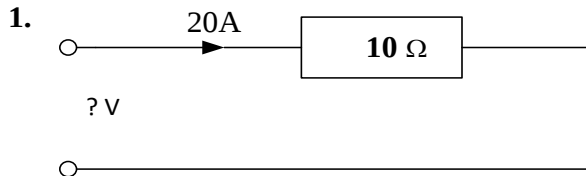
Determine the unknown value(s).
Layout your workings on another page.




Answer = Volts

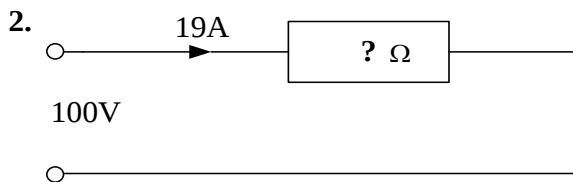


Answer = Ohms

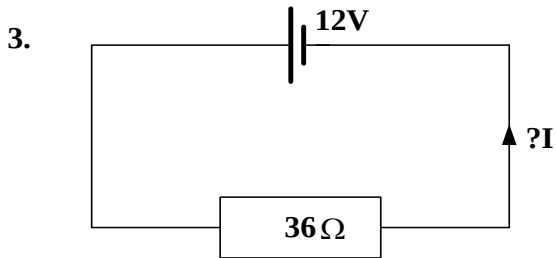

Answer = Amps

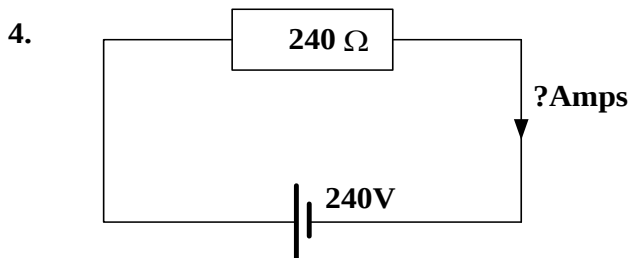

Answer = Amps

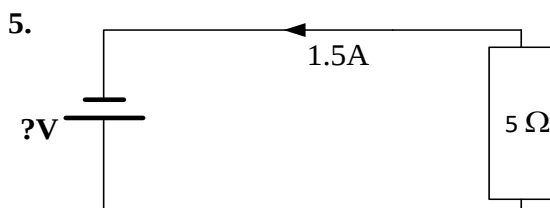

Answer = Volts

6. Fill in the gaps - use the triangle above to help.

Volts	Ohms	Amps
25	10	
45	5	
1.5	1	
	6	12
	100	10
	7	8
160		2
60		30
27		9
	50	4
18		10
19	37	

7. A. If the Resistance in a circuit is increased and the Voltage remains constant, Does the Current increase or decrease?

B. If the Voltage to a circuit increases and the Resistance remains constant, does the Current increase or decrease?


C. If the Resistance to a circuit is doubled, then what has happened to the Voltage?

Ohms Law.

Work Sheet 1B


Basic calculations.

Fill out this triangle now

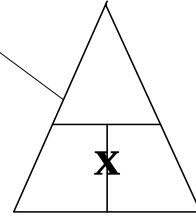


Determine the unknown value(s).


Layout your workings on another page.

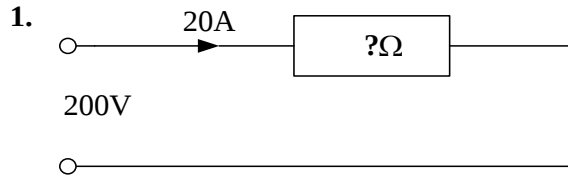


Answer = **Ohms**

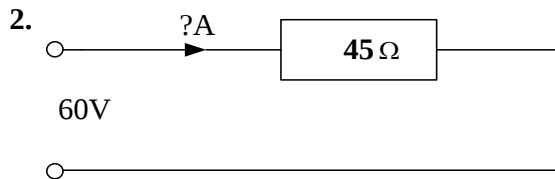

Answer = **Amps**

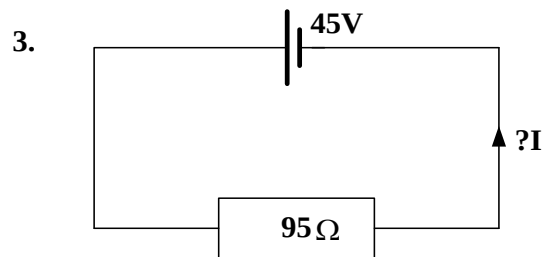

Answer = **Amps**

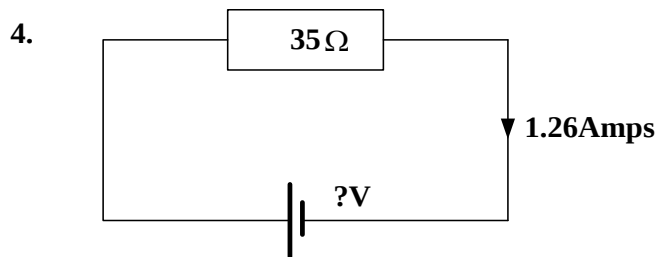


Answer = **Volts**




Answer = **Volts**

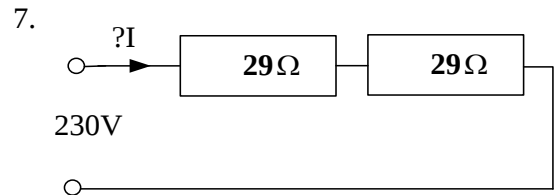
6. Now go and read your notes on series circuits characteristics. Write one of them below:



Answer = **Amps**

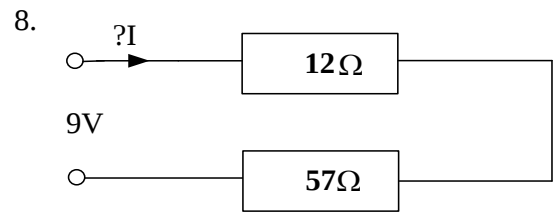

Answer = **Amps**

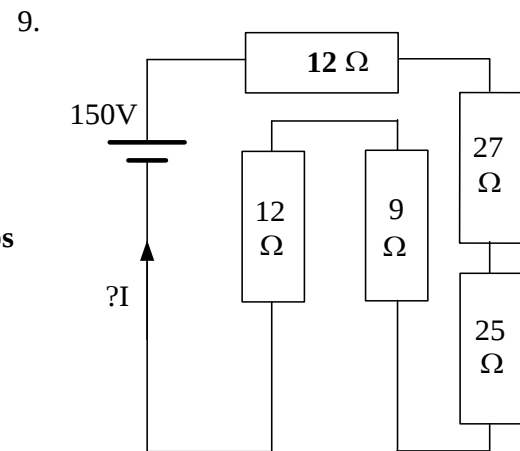



Answer = **Amps**

10. State Ohms Law in words:


Ohms Law. **Work Sheet 1C** **Basic calculations.**

Determine the unknown value(s).
Do all workings on another page


Fill out this triangle now

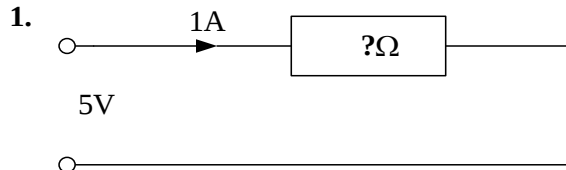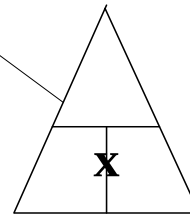


Answer = **Ohms**

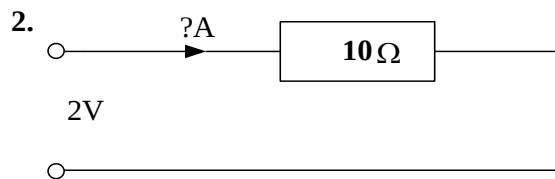


Answer = **Amps**

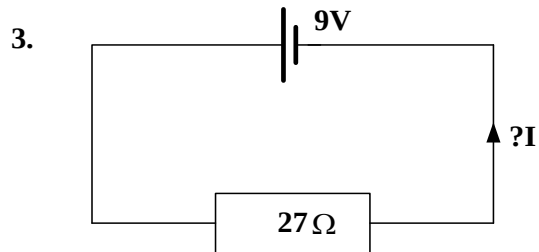

Answer = **Amps**

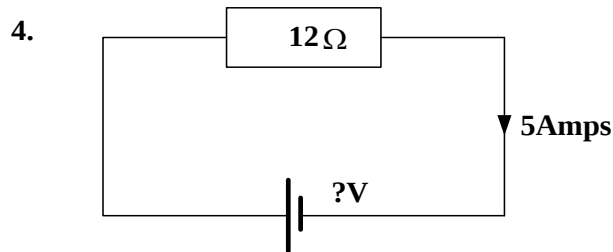


Answer = **Volts**

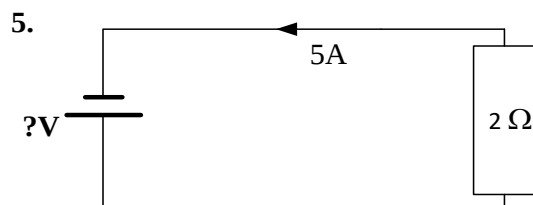

Answer = **Volts**


6. Now go and read your notes on series circuits characteristics.

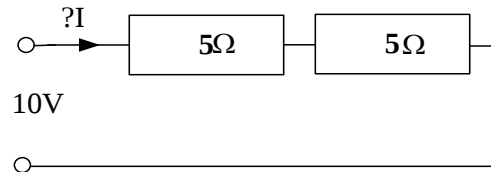7. To find total resistance, add together each series resistance.




Answer = **Amps**

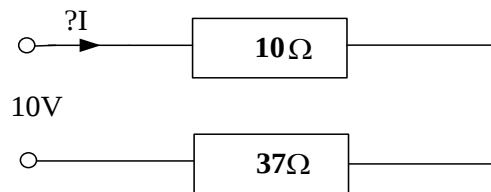8. To find total resistance, add together each series resistance.



Answer = **Amps**

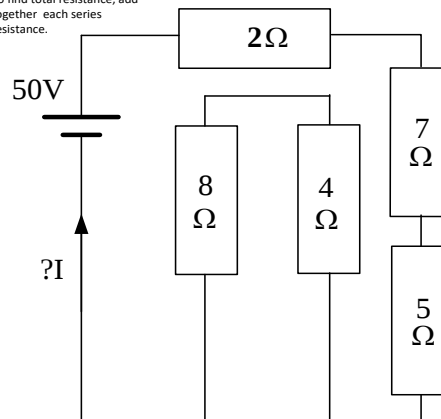9. To find total resistance, add together each series resistance.




Answer = **Amps**


10. Draw the symbol for a Battery Cell, show polarity. Is the current shown on these drawings Conventional current flow or electron flow?.

Ohms Law. Work Sheet 2A Series calculations.


Fill out this triangle now

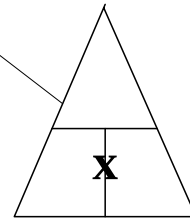

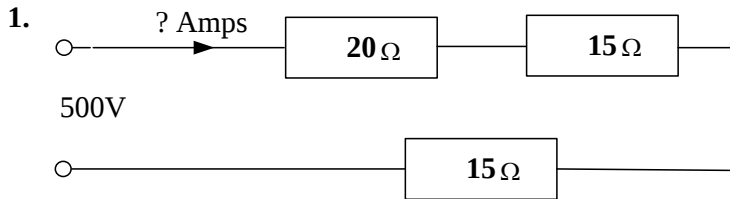
Determine the unknown value(s).
Layout your workings on another page.




Answer = Amps

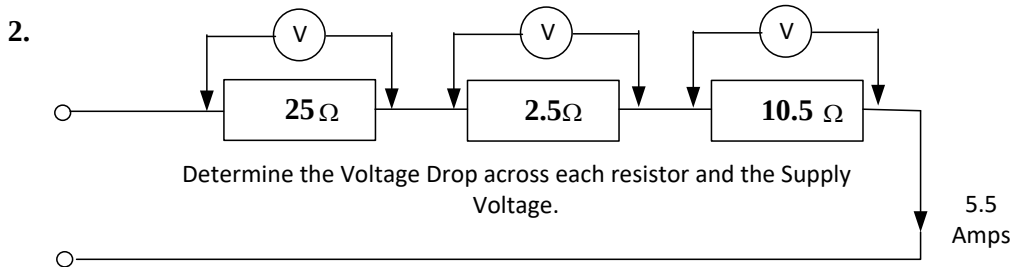

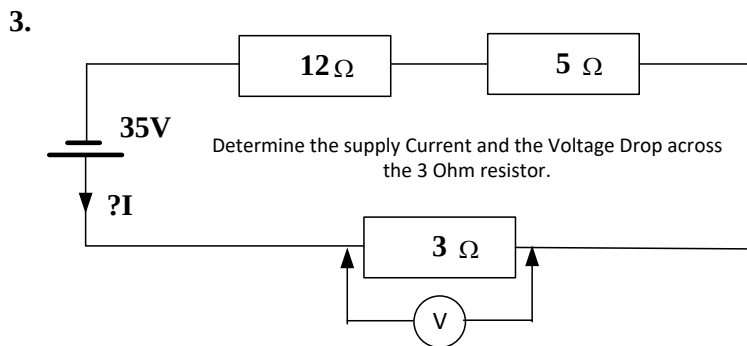
Answers: $V_{25} =$ $V_{2.5} =$ $V_{10.5} =$
 $V_s =$



Answers: $I_s =$ $VD_3 =$

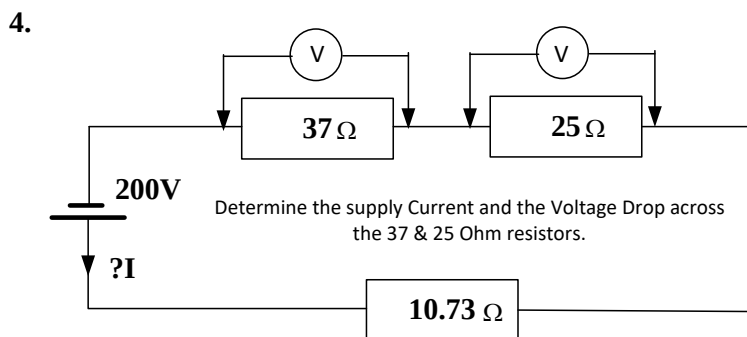


Answers: $I_s =$ $VD_{37} =$ $VD_{25} =$

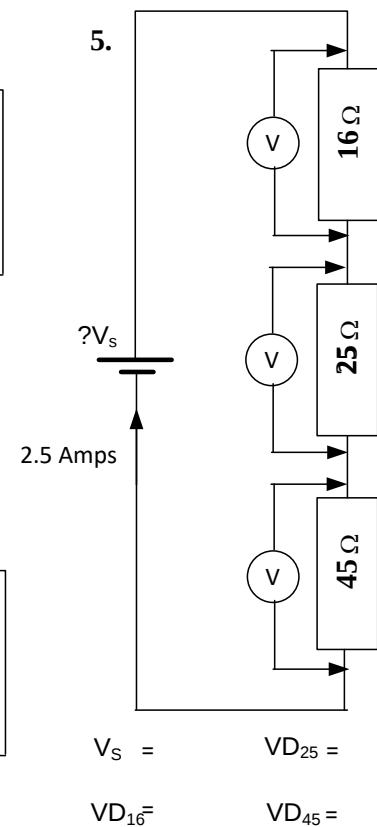


Ohms Law. Work Sheet 2B Series calculations.


Fill out this triangle now

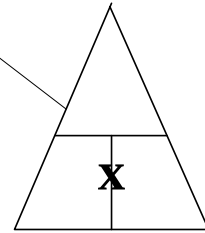

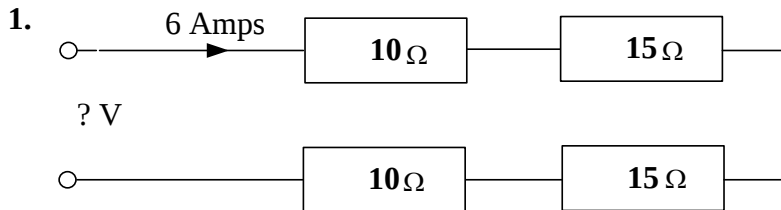
Determine the unknown value(s).
Layout your workings on another page.



Answer = Volts

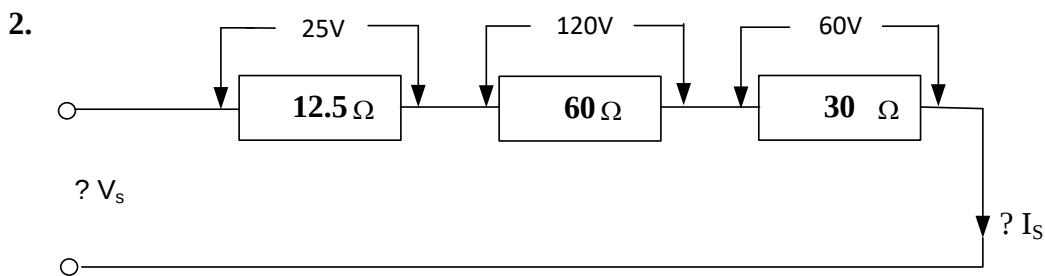

Answers: $V_s =$ Volts $I_s =$ Amps

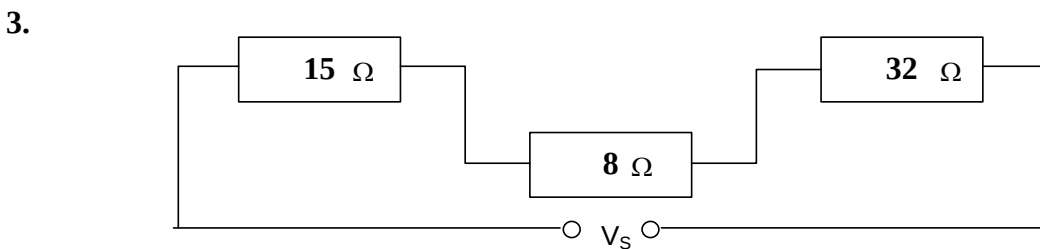

Determine the total current flow if
the Supply Voltage (V_s) is:

a. 10 Volts
 $I =$



b. 50 Volts. $I =$

4. Four resistors are connected in series. Each resistor has a resistance of 15 Ohms. If the supply Voltage is 100 Volts, what is the current drawn from the supply and what Voltage Drop would be measured across each resistor. Draw the circuit below (neatly) and show on it your calculated answers.


Determine the ? value(s).
Layout workings on another sheet

Ohms Law. **Work Sheet 3A** **Hard Series calculations.**

Fill out this triangle now

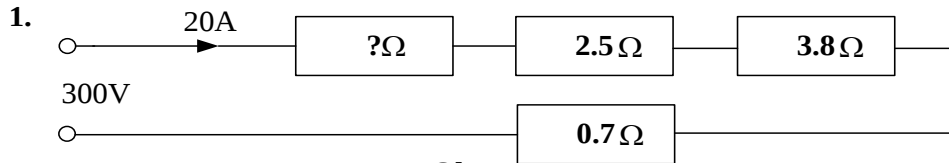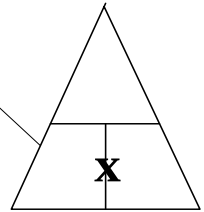


Answer: $R_?$ = Ohms

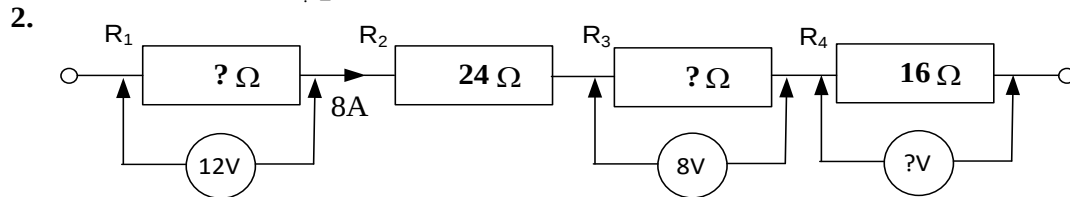


Answers: R_1 = R_3 = V_{R4} =

Supply Voltage =

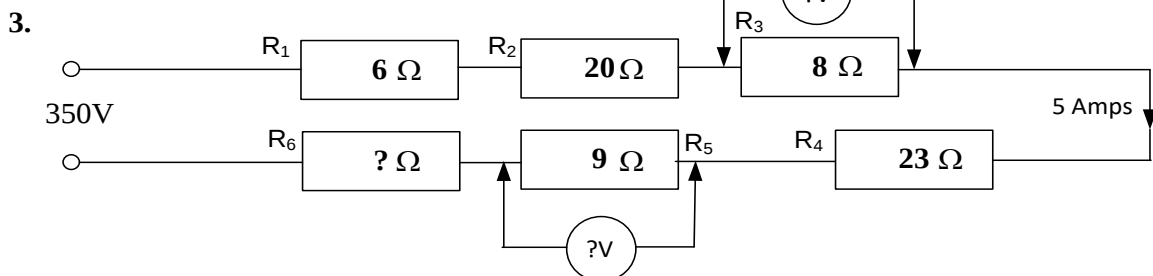


Answers: R_6 = V_{R3} = V_{R5} =

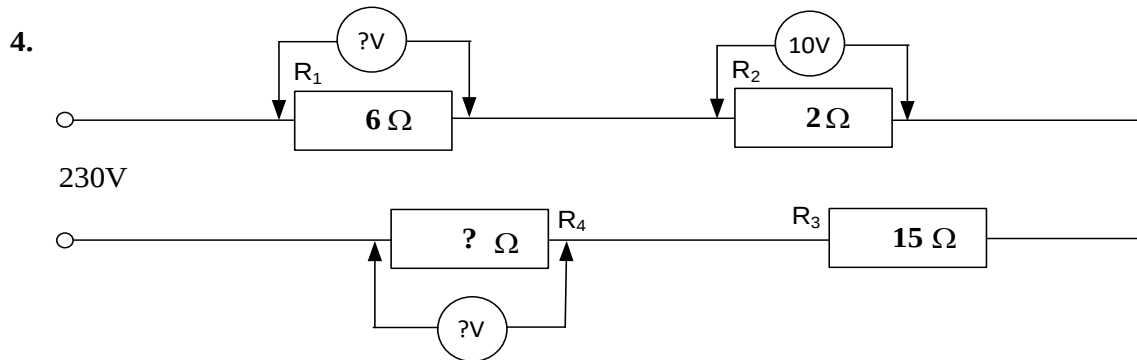

Answers: V_{R1} = V_{R4} = R_4 =

Total Current =

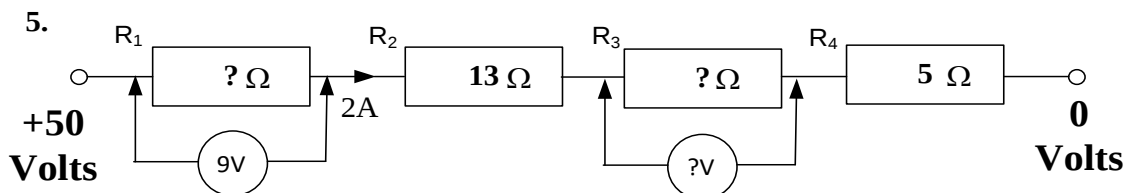


Answers: R_1 = R_3 = V_{R3} =

Ohms Law.


Work Sheet 5A

Basic Parallel calculations.

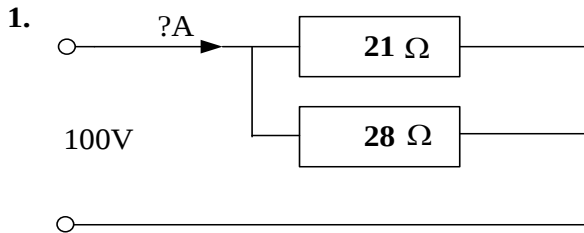
Determine the unknown value(s).
Layout your workings on another page.



Answer = **Amps**


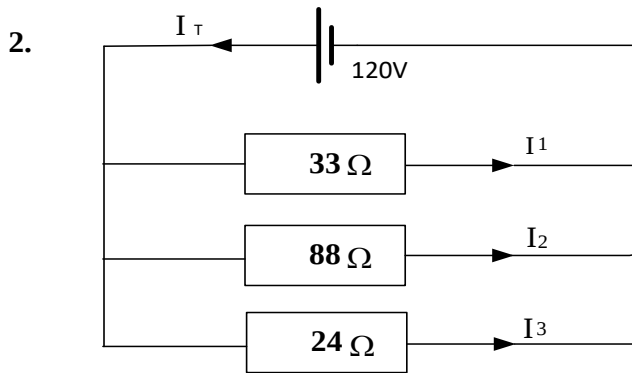


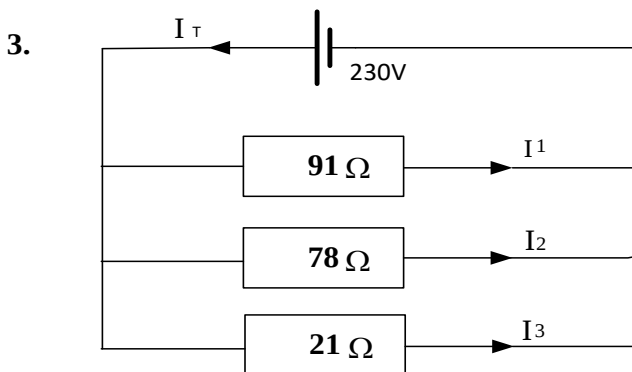Answers: $I_T =$
 $I_1 =$
 $I_2 =$
 $I_3 =$




Answers: $I_T =$
 $I_1 =$
 $I_2 =$
 $I_3 =$

Fill out this triangle now

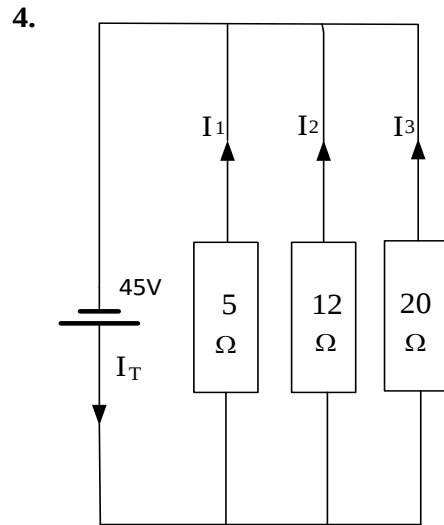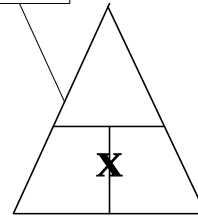

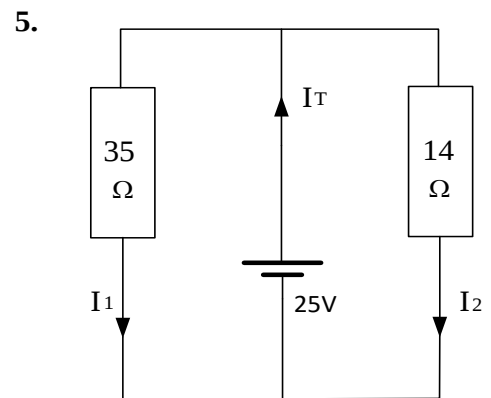Answers: $I_T =$
 $I_1 =$
 $I_2 =$
 $I_3 =$




Answers: $I_T =$
 $I_1 =$
 $I_2 =$

Ohms Law.


Work Sheet 6A

Harder Parallel calculations.

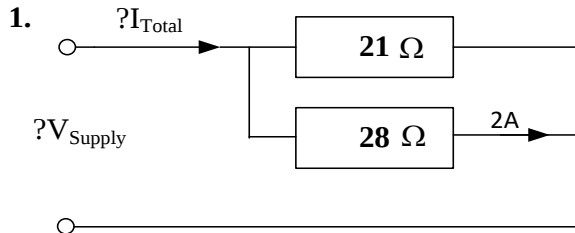
Determine the unknown value(s).
Layout your workings on another page.



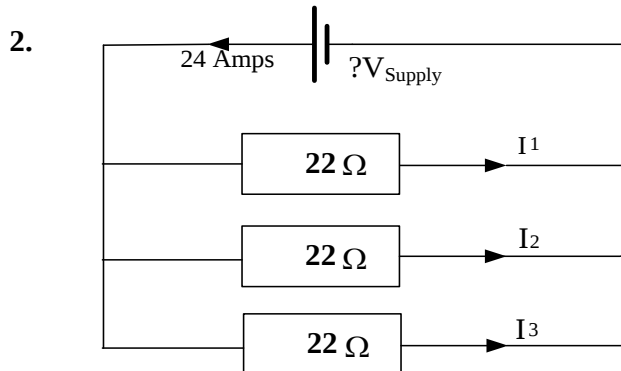
Answers : $I_{Total} =$ Amps. $V_{Supply} =$ Volts



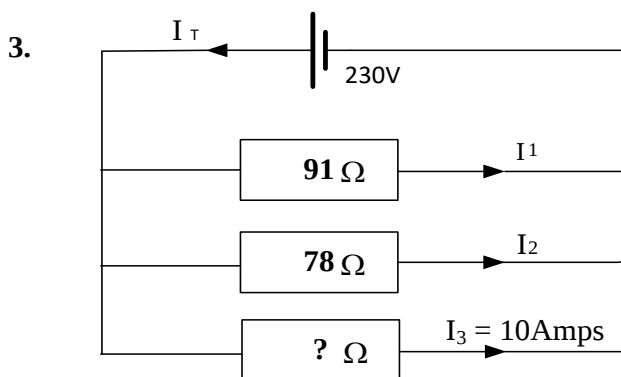
Answers: $I_1 =$
 $I_2 =$
 $I_3 =$
 $V_{Supply} =$



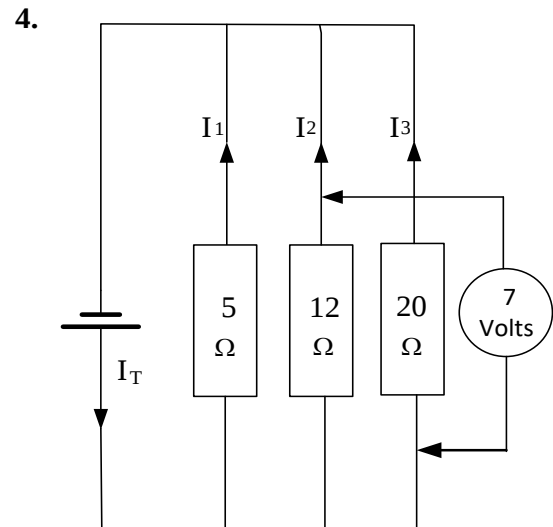
Answers: $I_T =$ Amps
 $I_1 =$ Amps
 $I_2 =$ Amps
 $R_3 =$ Ohms



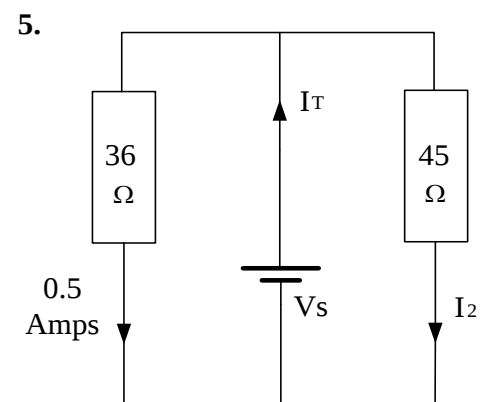Answers: $I_1 =$
 $I_2 =$
 $I_3 =$
 $I_T =$
 $R_T =$




Answers: $I_2 =$
 $I_T =$
 $V_S =$

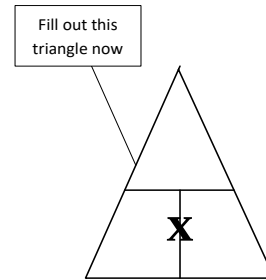


Find the total resistance for each network.

Work Sheet 10A


Total Resistance Network

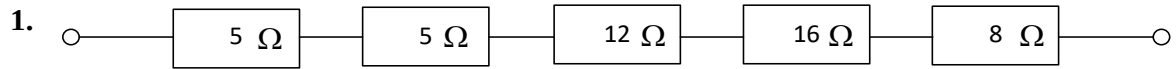


Answer = Ohms

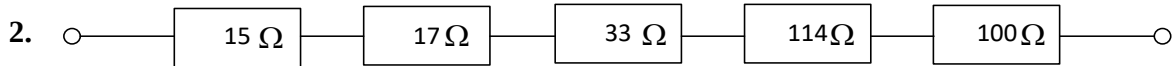


Answer = Ohms

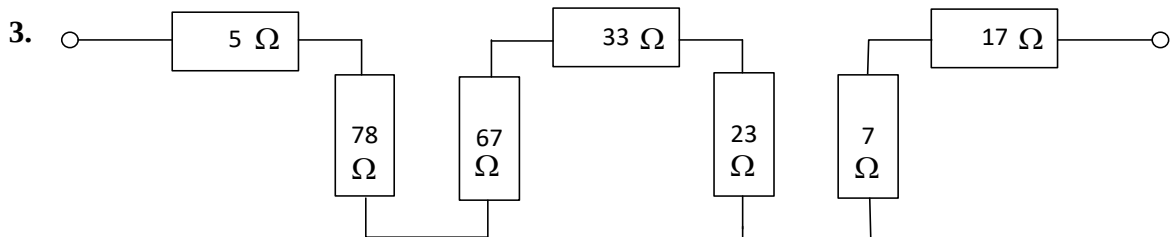

Answer = Ohms

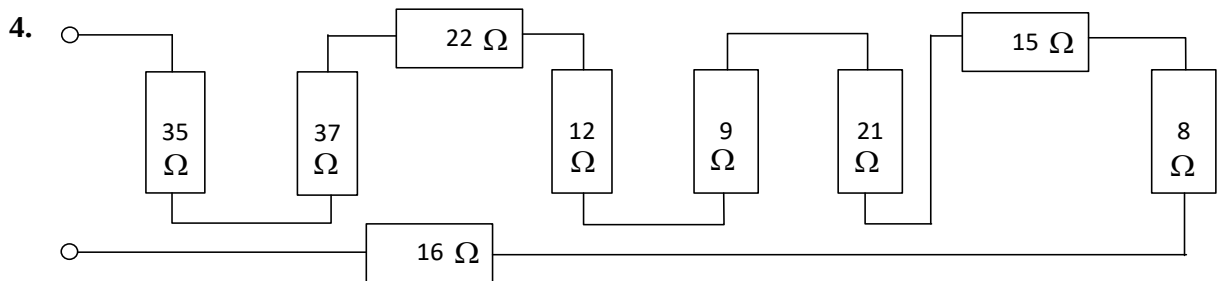

Answer = Ohms

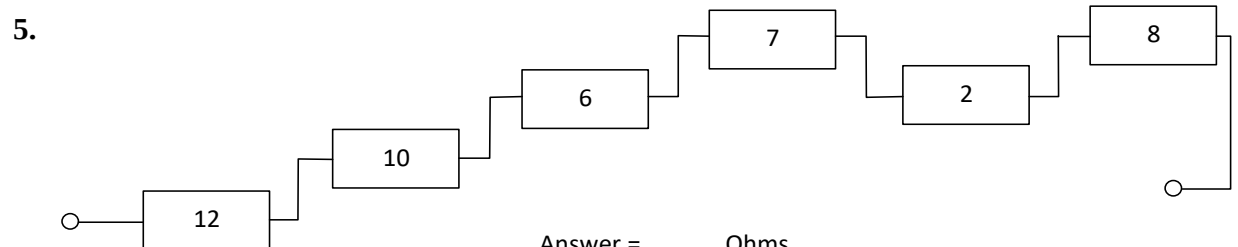


Answer = Ohms

6. Six 15 Ohm, three 10 Ohm and two 8 Ohm resistors are connected in series in a random order. Draw the circuit and calculate the total resistance.


Answer = Ohms

Find the total resistance for each network.


Work Sheet 10B Total Resistance Network

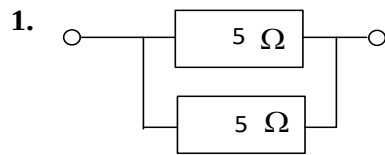


Answer = Ohms

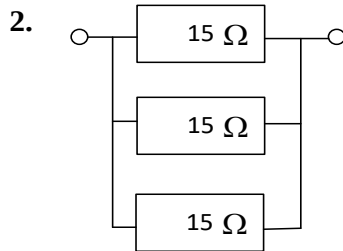


Answer = Ohms

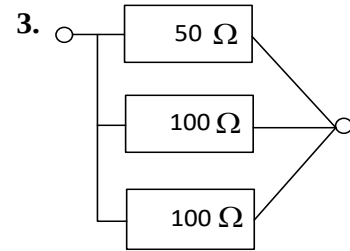


Answer = Ohms

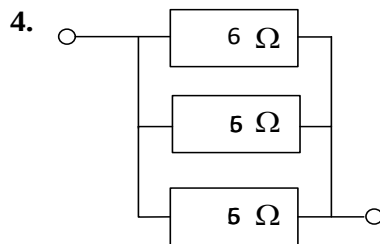


Answer = Ohms

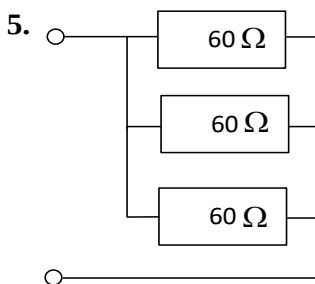


Answer = Ohms

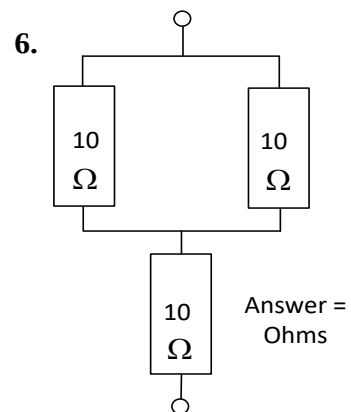


Answer =
Ohms

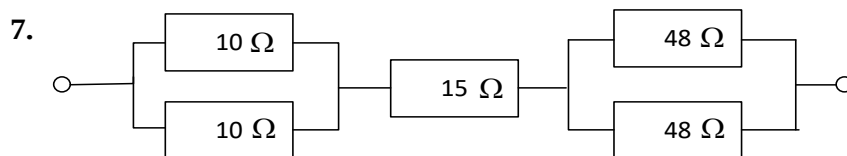

Answer = Ohms

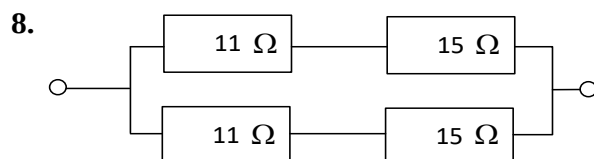

Answer = Ohms





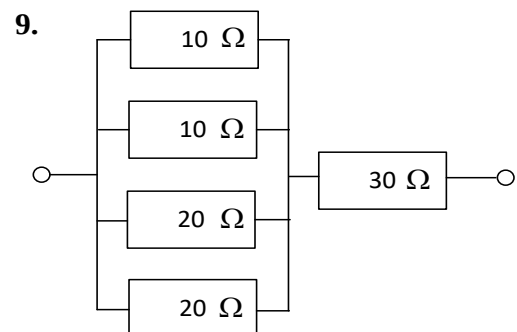


Answer = Ohms

Find the total resistance for each network.

Work Sheet 10C

Total Resistance Network Calcs

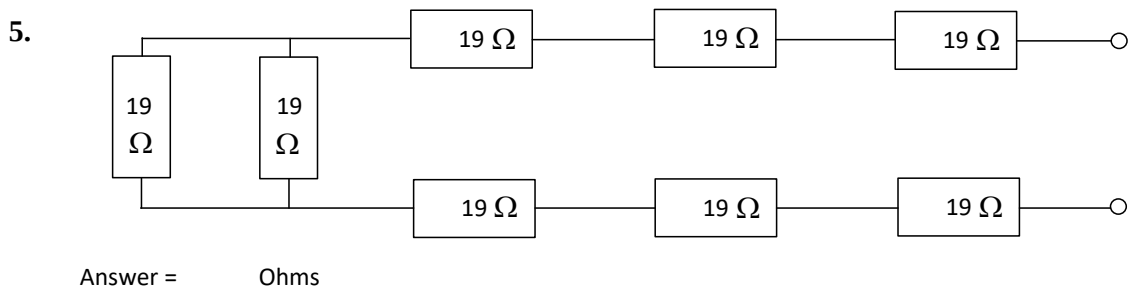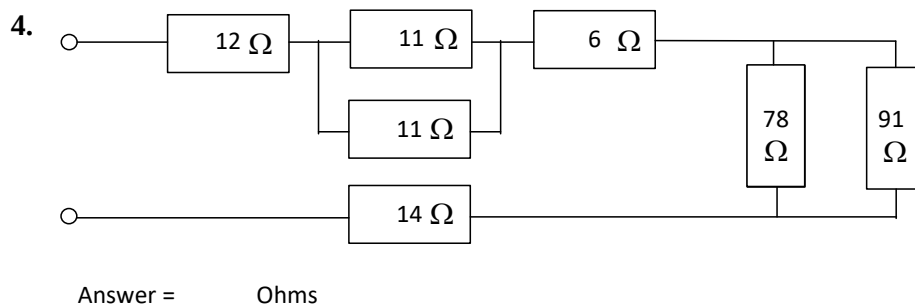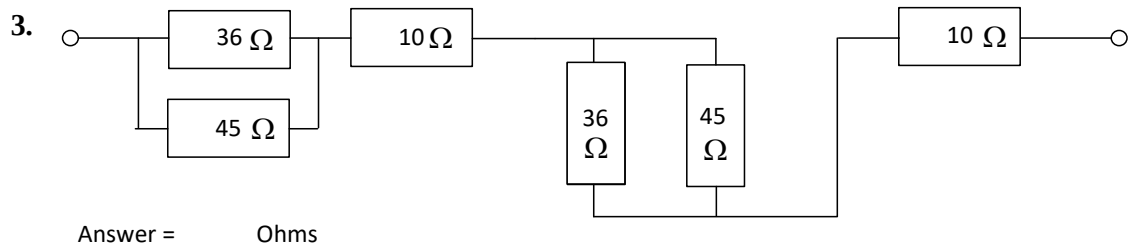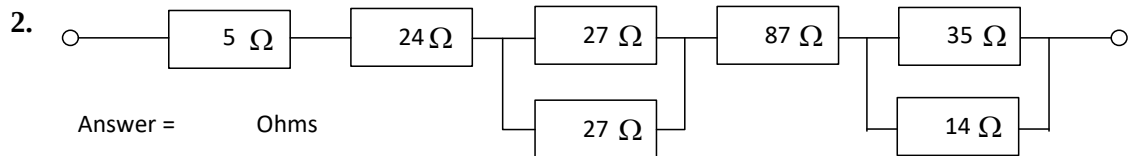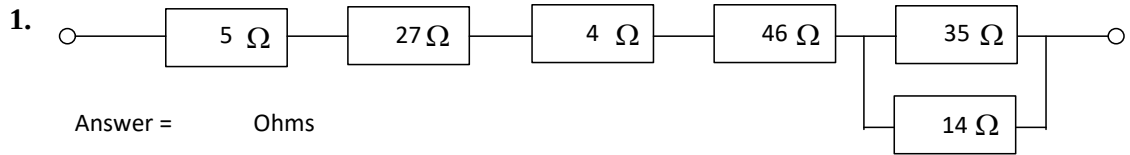


6. Three 27 Ohm resistors are connected in series and then two 5 Ohm resistors in parallel are also connected in series. Draw the circuit and find the total resistance in ohms.

Answer = Ohms


Find the total resistance for each network.

Work Sheet 10D


Total Resistance Network Calcs

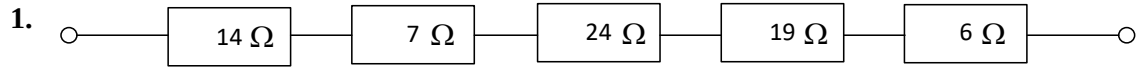


Answer = Ohms

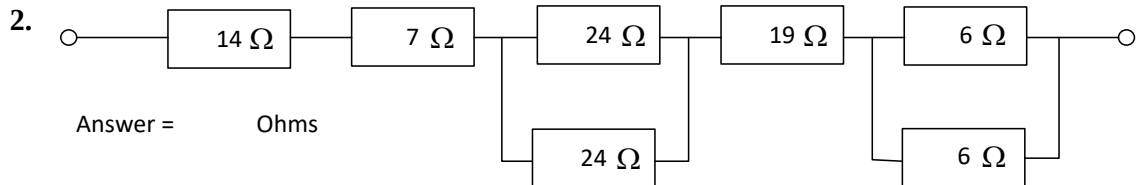


Answer = Ohms

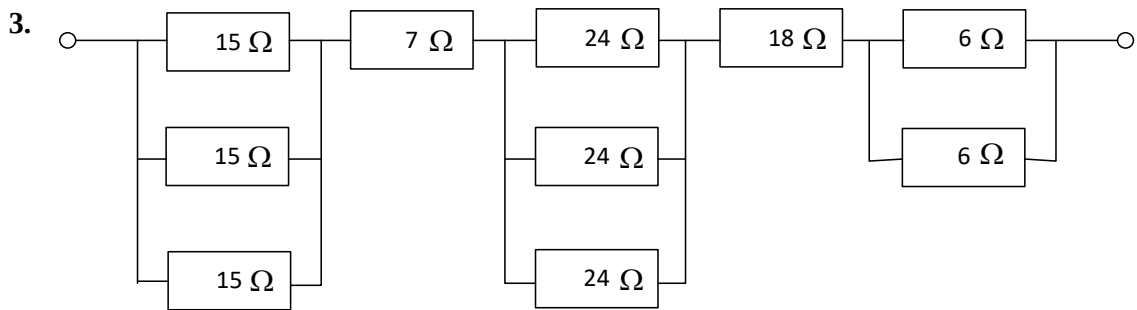

Answer = Ohms

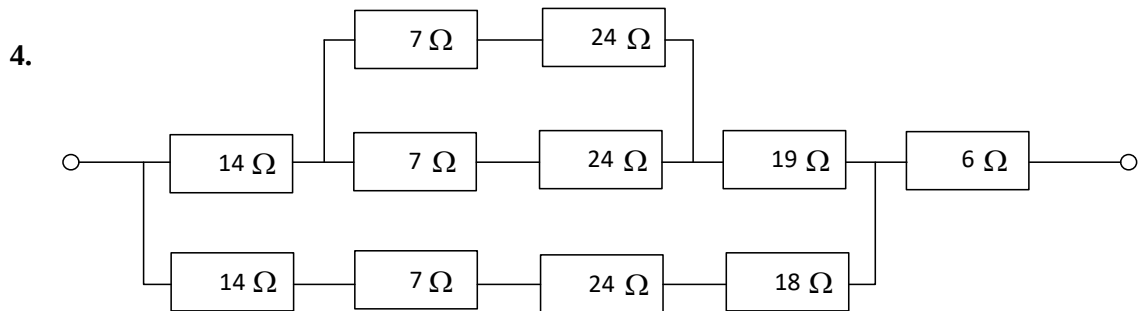

Answer = Ohms

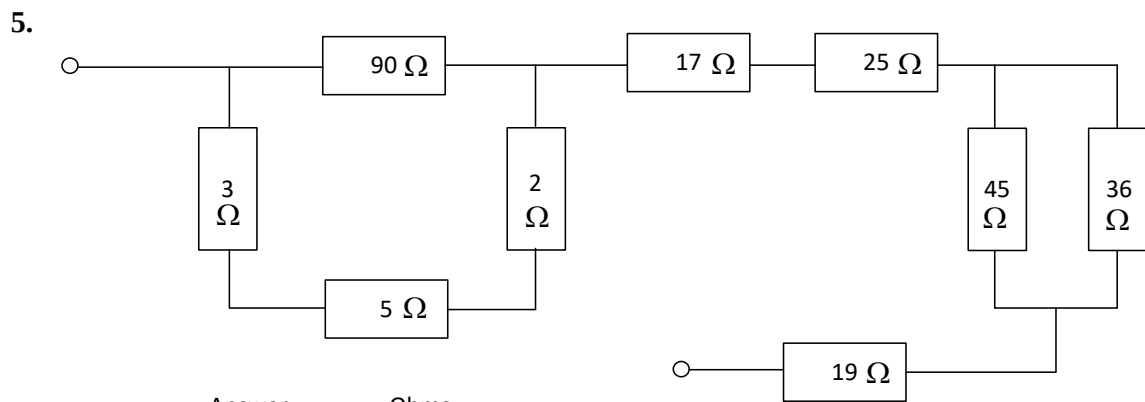


Answer = Ohms


Find the total resistance for each network.

Work Sheet 11A


Total Resistance Network Calcs - Harder

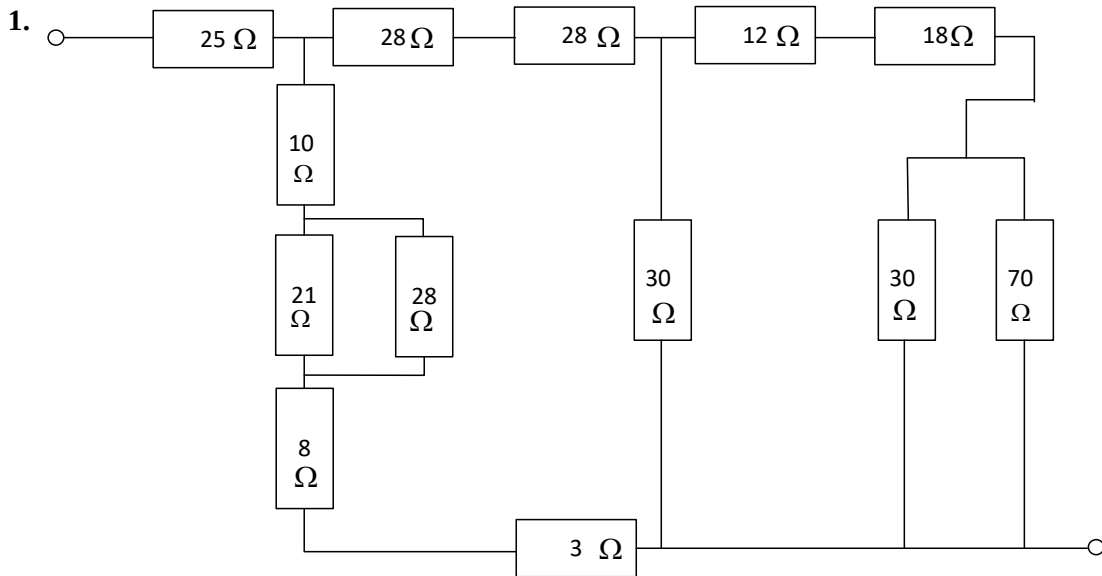

Answer = Ohms

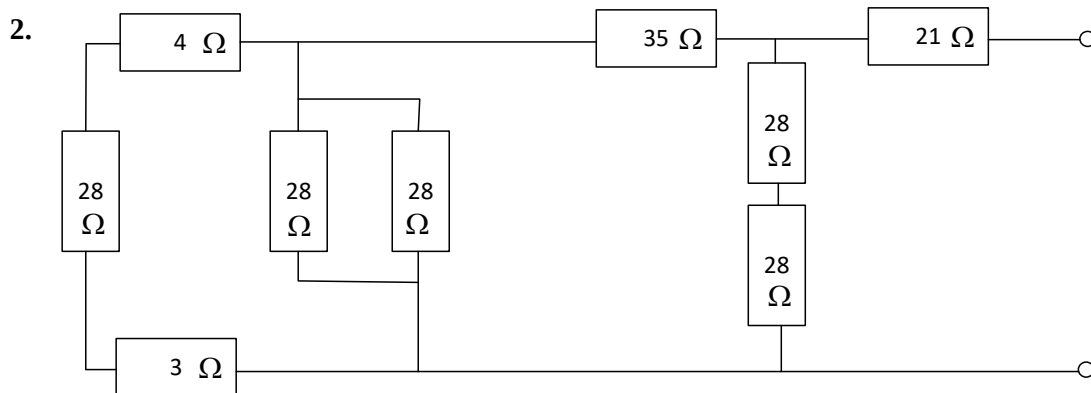

Answer = Ohms



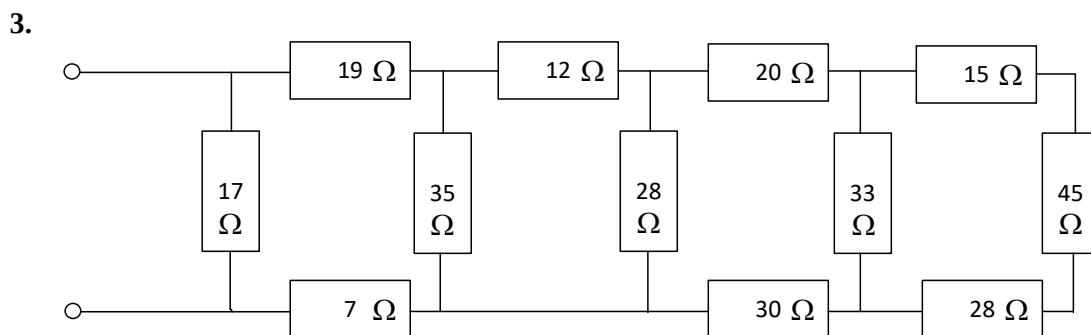


Answer = Ohms


Find the total resistance for each network.

Work Sheet 11B






Total Resistance Network Calcs - Harder

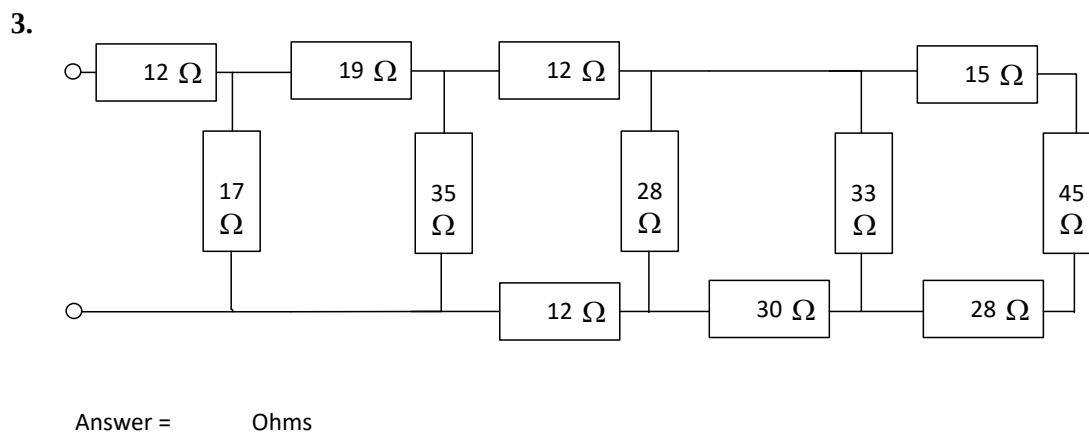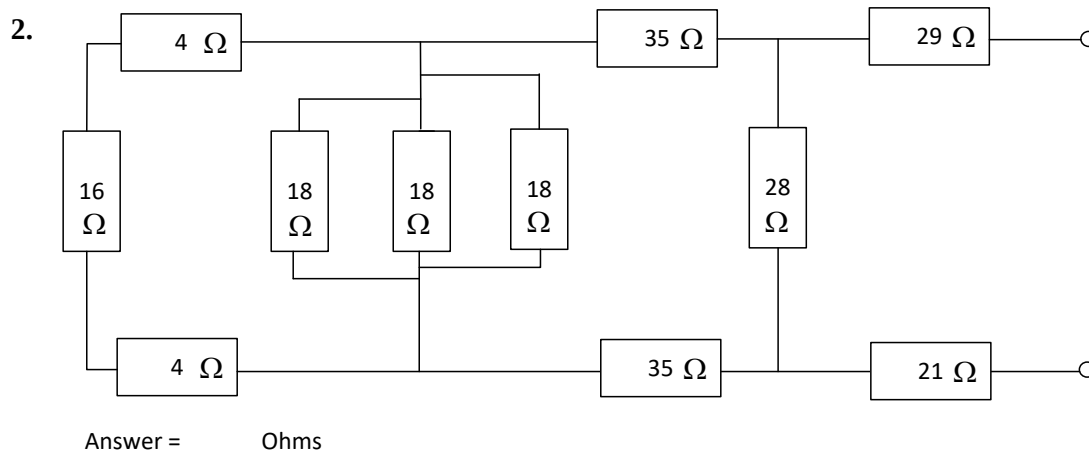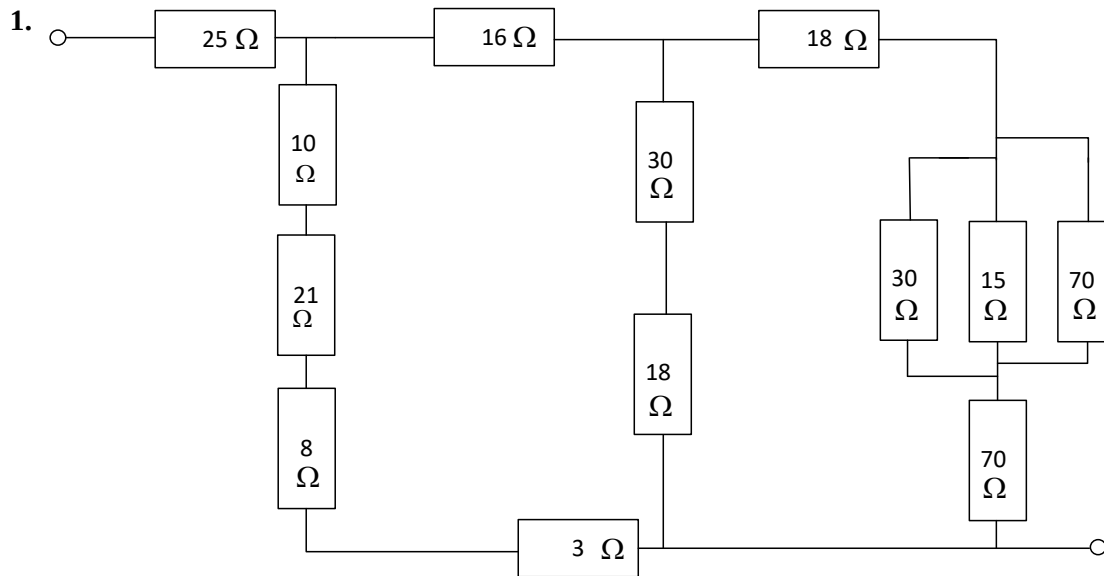

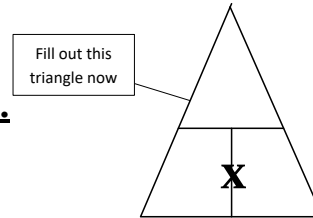Ohms Law. **Work Sheet 15A** **Basic Series-Parallel calculations.**



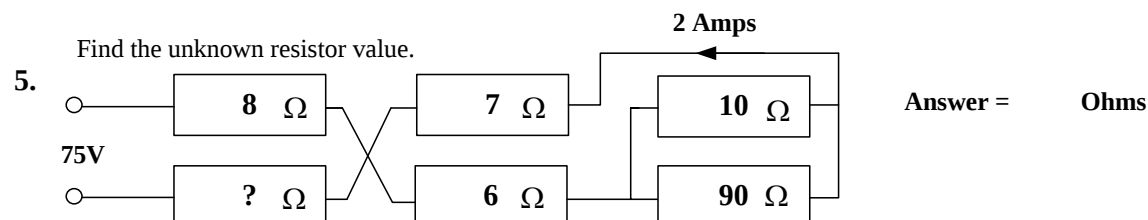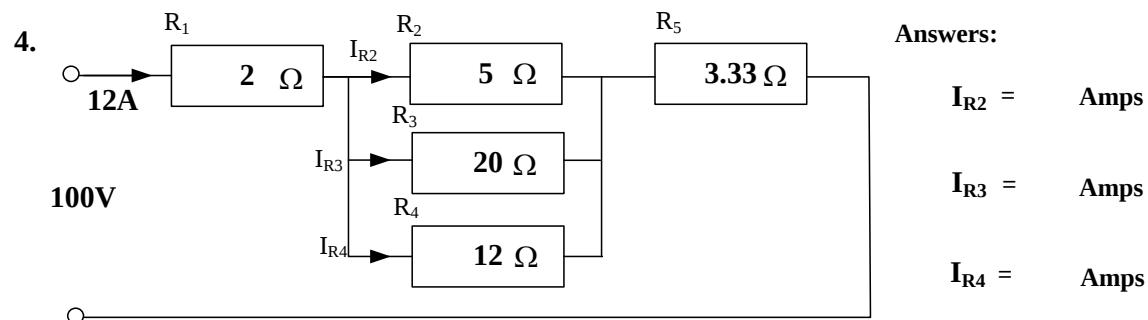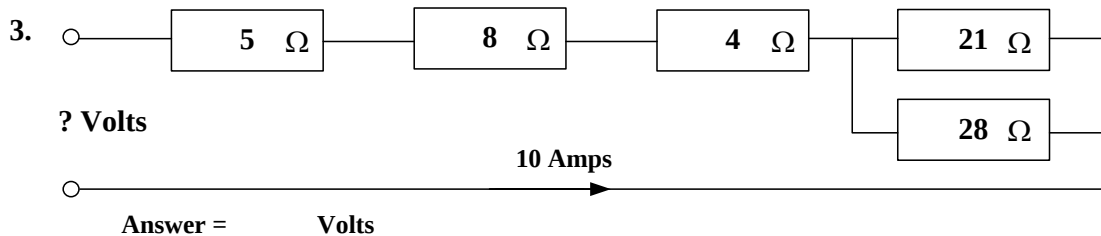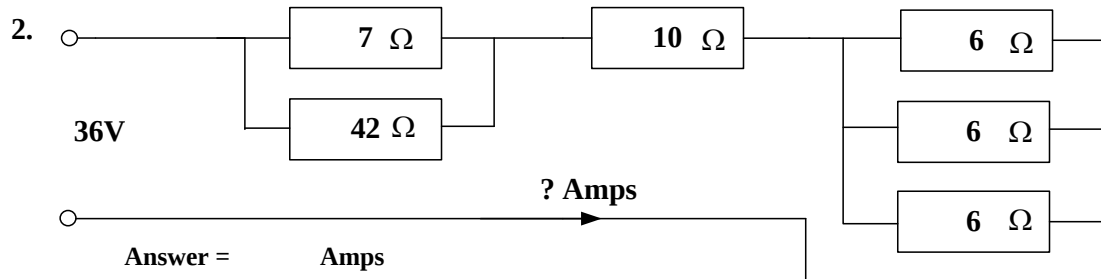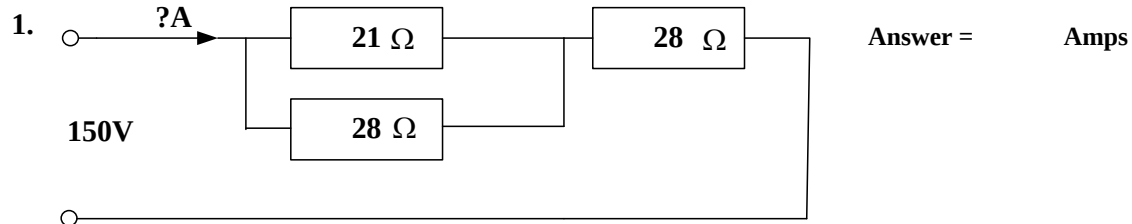
Determine the unknown value(s).
 Layout your workings on another page.








Ohms Law.

Work Sheet 15B

Basic Series-Parallel calculations.

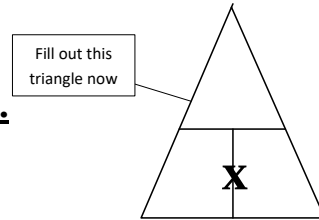

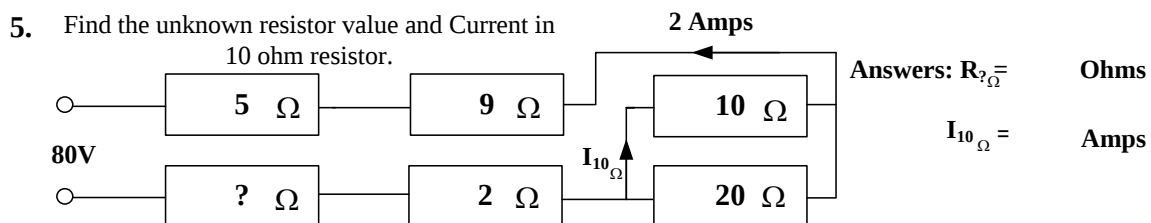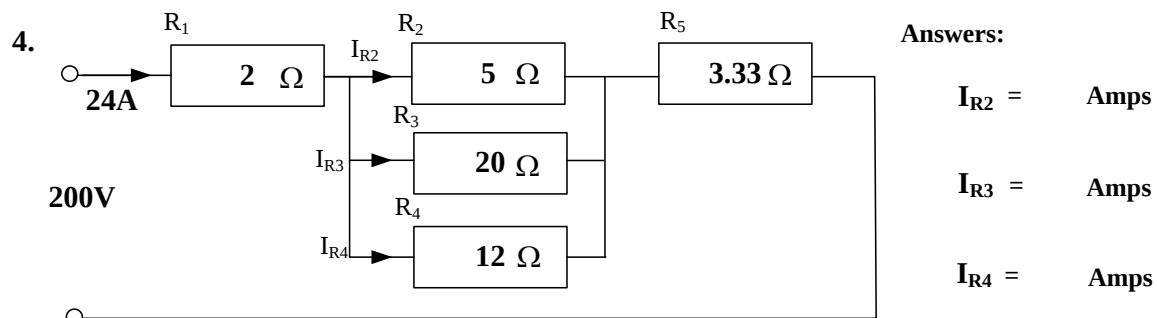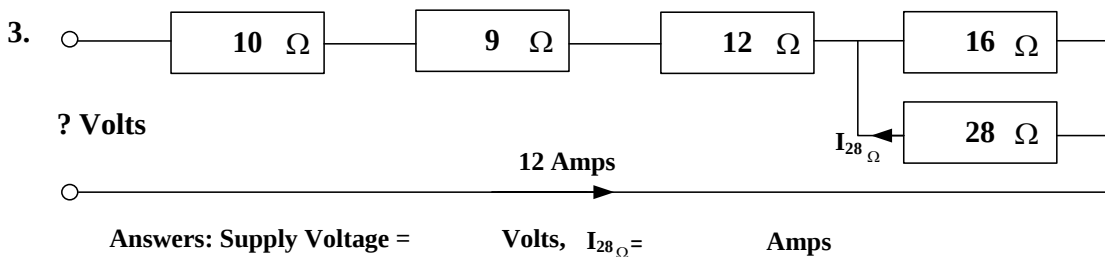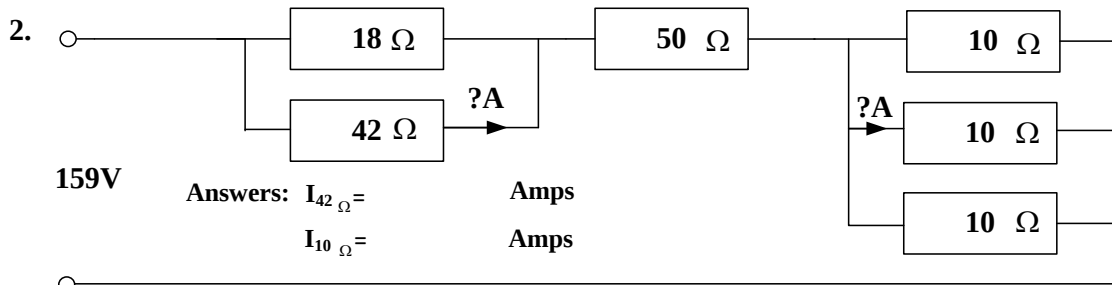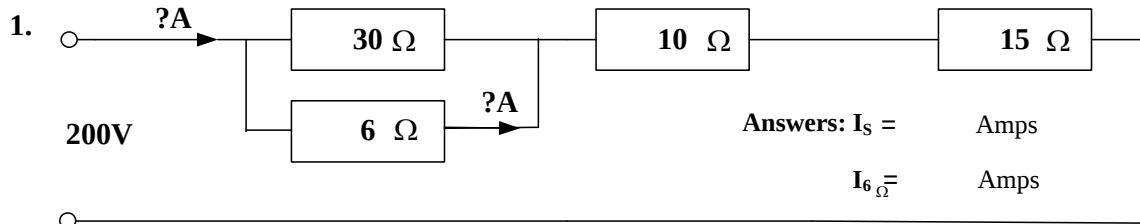Determine the unknown value(s).
Layout your workings on another page.



Work Sheet 8 A.

Series and Parallel problems - Words.

For each problem DRAW the circuit, put the information from the question onto the drawing and then solve using - guess who's law.

1. Three resistors are connected in parallel and then this combination is connected in series with a 10 Ohm resistor. When 500 Volts is applied to the circuit, 25 Amps flows in the 10 Ohm series resistor. If 2 of the parallel resistors are 28 Ohms each then what is the value of the unknown resistor, and what is the current through it and the voltage drop across it ?
2. A heating element is in two sections, each of 45 Ohms. Find the current drawn from the supply (230V) when the sections are connected in a) series and b) parallel ?
3. Two cables having resistances of 0.5 Ohms and 0.8 Ohms carry between them a current of 30 Amps. What is the current in each cable and the Voltage Drop that occurs when the current is flowing ?
4. A cable carries a current of 45 Amps and when that happens a voltage drop of 21 Volts occurs. What would be the resistance value of a cable connected in parallel with the first to reduce the voltage drop to 5% of 230 Volts.
5. The specification for a wire to be used in a wire wound resistor says that its resistance is 0.6 Ohms per meter. How many meters would be required to give :
 a) A resistance of 3.7 Ohms, and
 b) 0.2 Ohms, given that the wire must be at least a meter long to reach from one end of the resistor to the other ?
6. A circuit consists of three resistors initially connected in series and then in parallel. What in general terms occurs to the following, given the changes listed.

Series

Parallel

Supply current:
if Voltage is doubled ?


Total resistance:
if one resistor is removed ?

Supply voltage :
if the current has halved ?


Total current:
if an extra resistor is added ?

Voltage drop across each resistor:
if an extra resistor is added ?




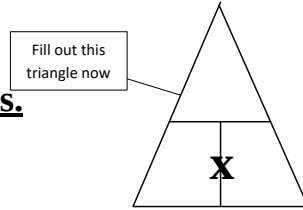
Ohms Law. **Work Sheet 16A** **Harder Series-Parallel calculations.**



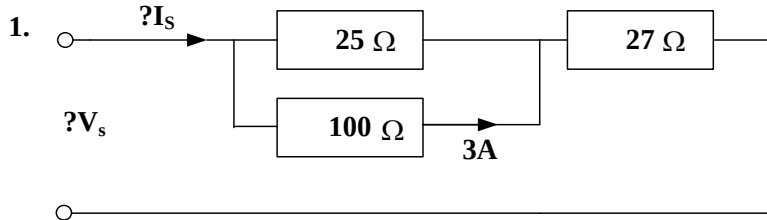Determine the unknown value(s).
 Layout your workings on another page.




Answers:
 $I_s =$ Amps
 $V_s =$ Volts

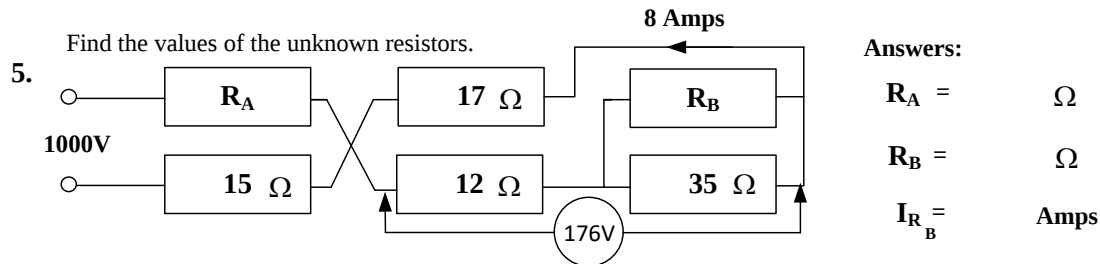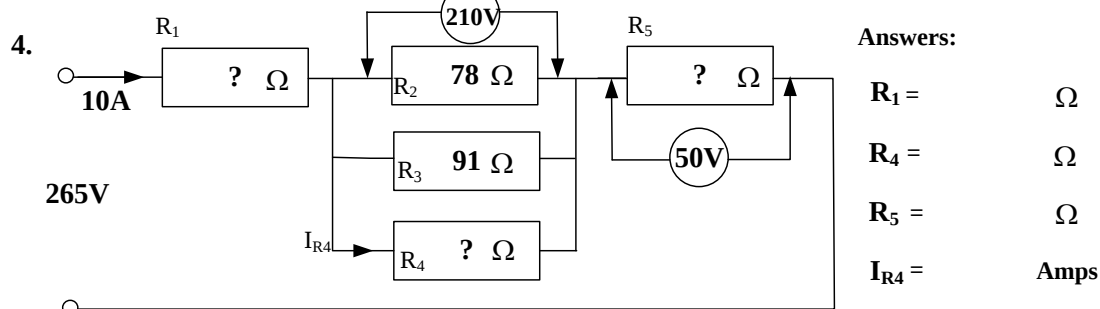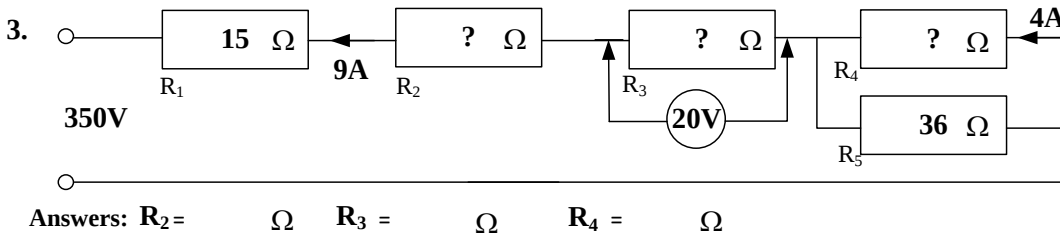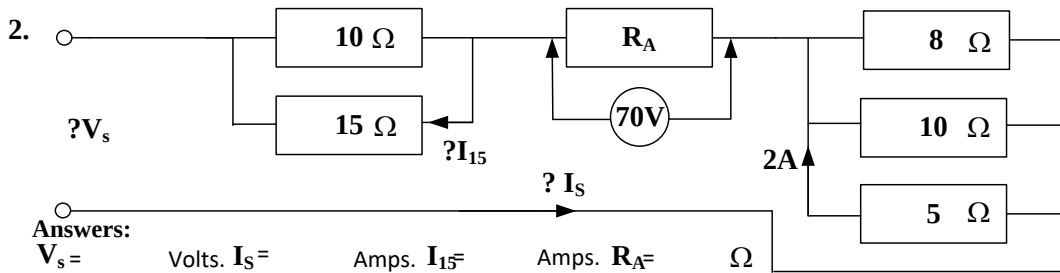

Ohms Law.
Work Sheet 16C
Harder Series-Parallel calculations.

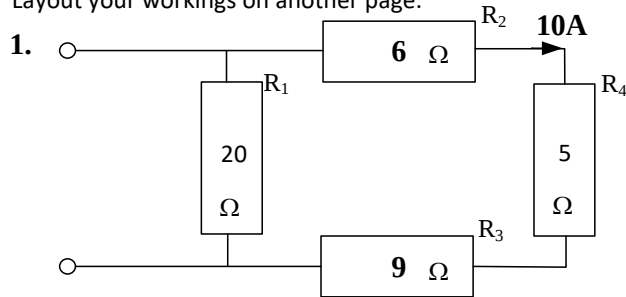
Determine the unknown value(s).
 Layout your workings on another page.



Answers:

$$V_s = \text{Volts}$$

$$I_{R1} = \text{Amps}$$

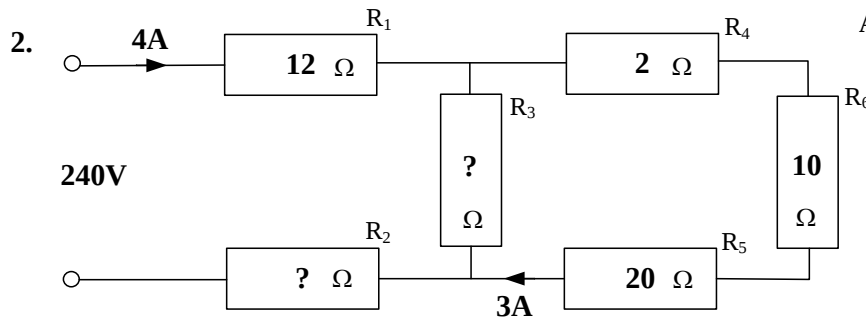


Answers:


$$I_{R3} = \text{Amps}$$

$$R_3 = \text{Ohms}$$

$$R_2 = \text{Ohms}$$

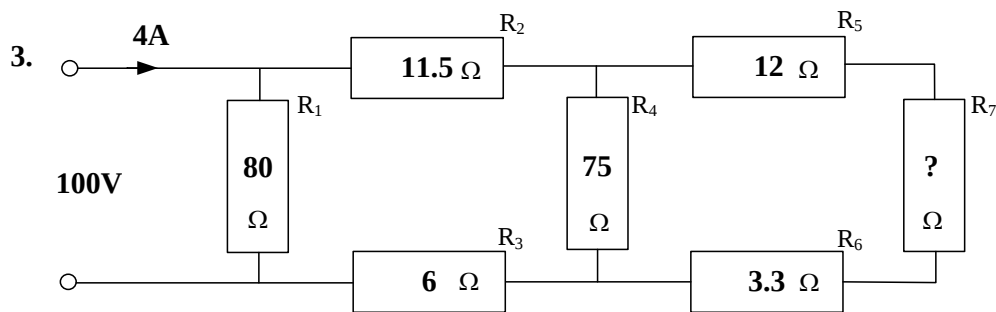

$$R_7 = \text{Ohms}$$

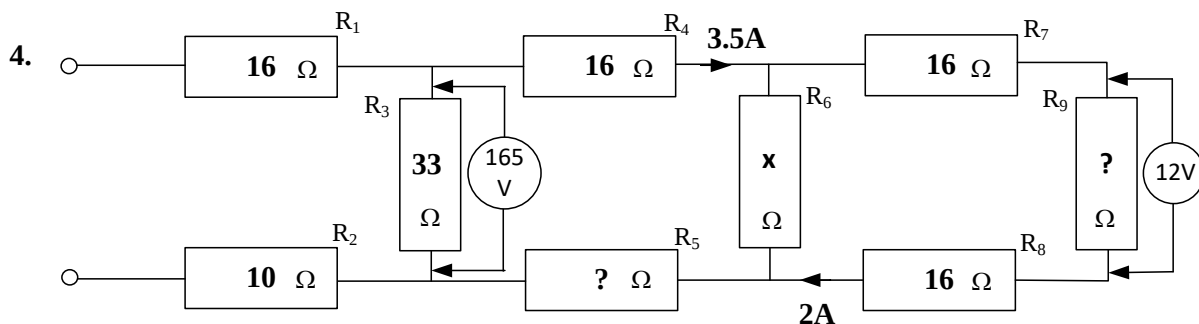


Find: $V_s =$ Volts, $R_T =$ Ohms, $R_9 =$ Ohms.

Internal resistance

25070E6


Every source of EMF, whether a cell/battery, power supply, generator or transformer has an internal resistance.

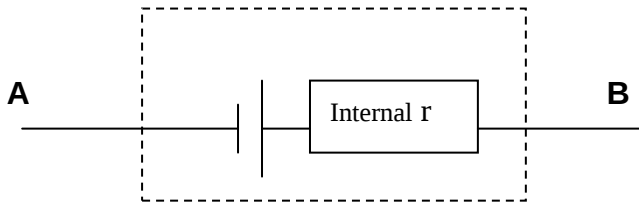This internal resistance has an effect on the final voltage available to do any work. As current is drawn, by ohms law, the voltage is reduced at the supply terminals. This can be illustrated by diagram below.



When the power supply is measured with no load attached we see an EMF available. This is measured across AB. No current is flowing and there is no volt drop across the internal resistance.

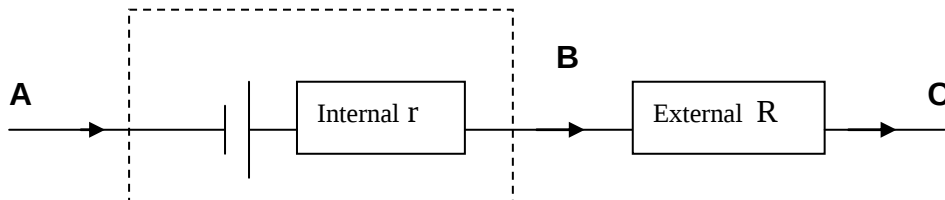When we connect a load, as shown below, a current is drawn. By ohms law a voltage will drop across the internal resistance and across the external load resistance. Some of the original EMF is “used up” inside the supply leaving less available for the external circuit.



By Kirchhoffs voltage law we see that; $V_{EMF} = V_{internal\ r} + V_{external\ load}$

For example:

2.3v is measured across the terminals of a lead acid cell with no load connected. The internal r is 0.1Ω . When 3A flows what is the voltage available at the cells terminals

Voltage at the terminal = EMF — Voltage internal
 Voltage internal = Supply current X internal resistance ($V = I \times R$)
 Therefore terminal voltage = $2.3v - (3A \times 0.1\Omega)$
 $= 2.0v$


This shows that 0.3v is dropped or lost inside the cell under this load.

Work Sheet 9A

Internal Resistance of a power supply - e.g. Battery.


The internal resistance is represented by a series resistor within the source.

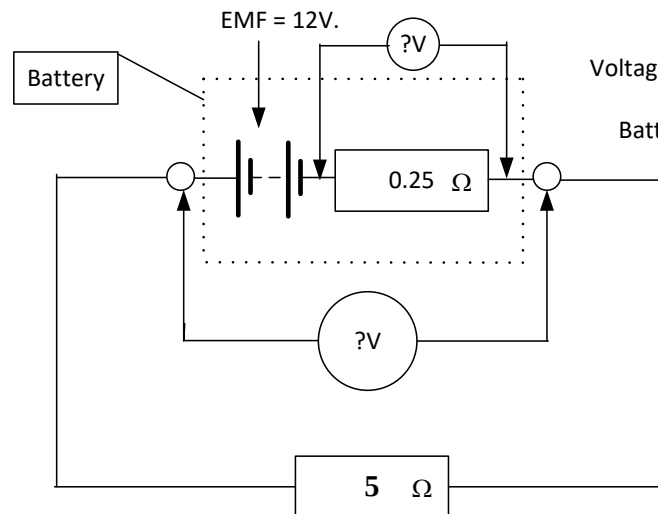1. A battery has an EMF of 12 V and an internal resistance of 0.25 Ohms.
Find the drop in voltage across the battery output terminals when a load of 5 Ohms is applied and the battery output Voltage?.



Answers:
Voltage Drop across internal resistance. = Volts.
Battery output Voltage. = Volts.

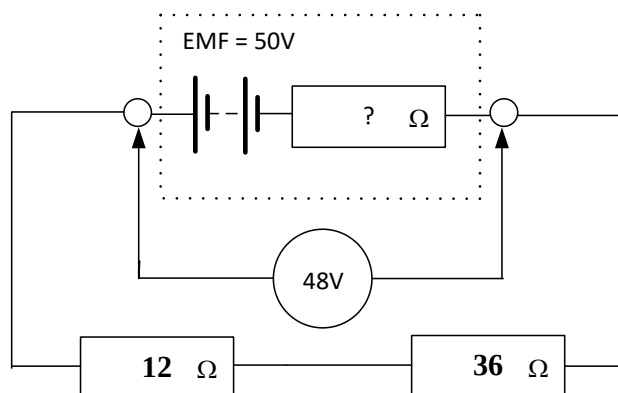2. Determine the value of the internal resistance?.




Answer = Ω

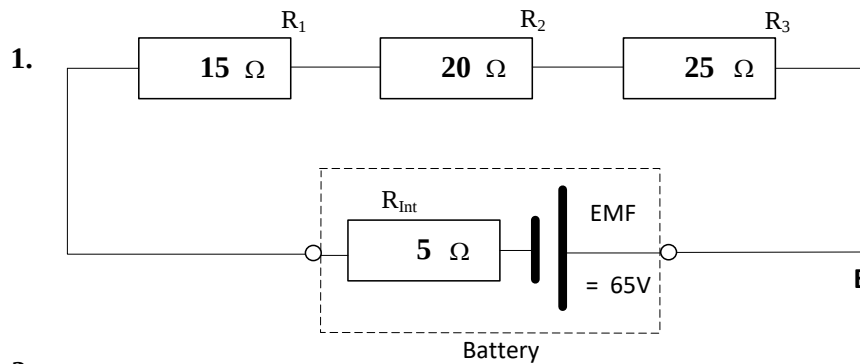3. Ten 1.5V cells are connected in series. Each cell has an internal resistance of 0.15 Ohms. What would be the Voltage across a 6 Ohm load resistor placed across the complete battery?. (Hint - Draw the circuit here)

Answer = Volts.

Ohms Law.
Work Sheet 16D
Harder Series-Parallel calculations.



Answers:

$V_{R1} =$ Volts


$V_{R2} =$ Volts

$V_{R3} =$ Volts

$V_{Int} =$ Volts


Battery output Voltage

$=$ Volts

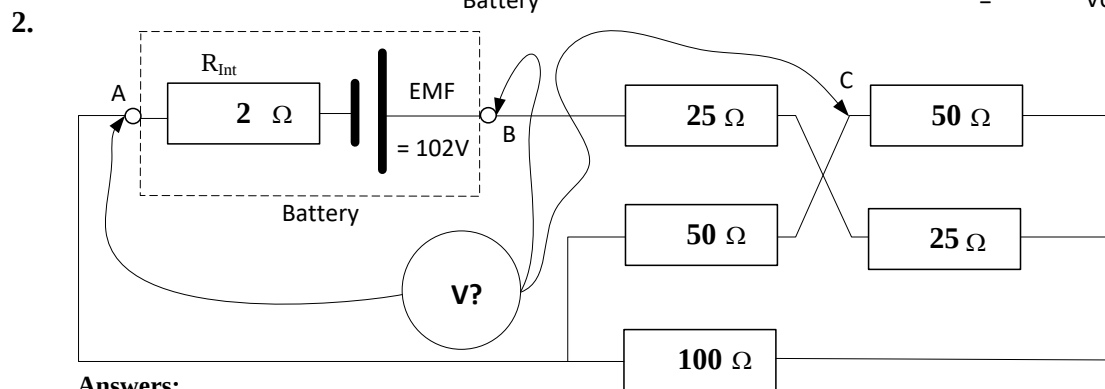

Answers:

$V_{A-B} =$ Volts $V_{A-C} =$ Volts

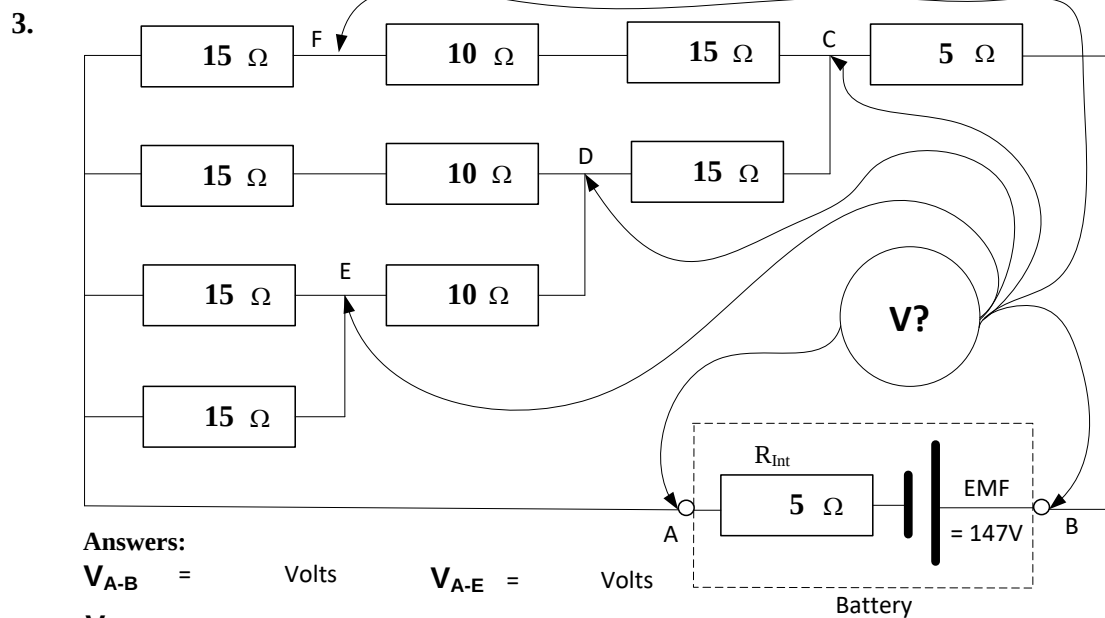

Answers:

$V_{A-B} =$ Volts


$V_{A-E} =$ Volts

$V_{A-C} =$ Volts

$V_{A-F} =$ Volts

$V_{A-D} =$ Volts

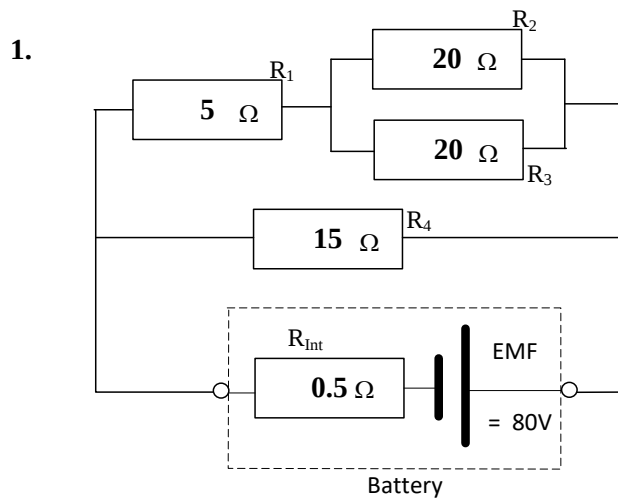Ohms Law.
Work Sheet 16E
Harder Series-Parallel calculations.



Find:

V_{R1} = Volts

V_{R2} = Volts

I_{R3} = Amps


Battery output Voltage

= Volts


2. If the current through R_2 is 7.5 Amps, find:

The EMF produced by the Battery

= Volts

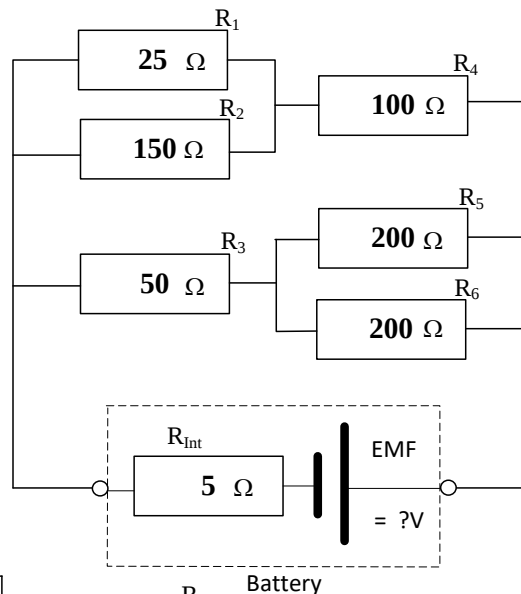

3.

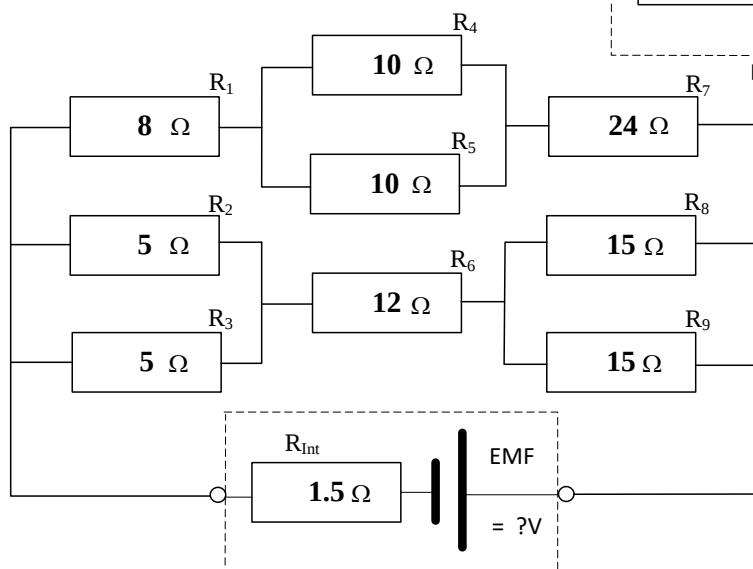

If the Voltage measured across R_5 is 32 Volts, find:

The EMF produced by the Battery

= Volts &,

The Potential Difference that would be measured across R_6

= Volts

Kirchhoff answers

These answers are listed to enable you to check if you have correctly solved the questions asked. If you cannot solve a particular problem ask your tutor for assistance. All answers must show line by line working before they will be signed off as completed.

- 1A) **1/** 200v **2/** 5.26 Ω **3/** 0.33A **4/** 1A **5/** 7.5v
6/ 2.5, 9, 1.5, 72, 1000, 56, 80, 2, 3, 200, 1.8, 0.514
7a/ decrease **7b/** increase **7c/** doubled if current kept the same
- 1B) **1/** 10 Ω **2/** 1.33A **3/** 0.47A **4/** 44.1v **5/** 225v **6/** see tutor
7/ 3.97A **8/** 0.13A **9/** 1.76A **10/** see tutor
- 1C) **1/** 5 Ω **2/** 0.2A **3/** 0.33A **4/** 60v **5/** 10v **7/** 1A **8/** 0.213A
9/ 1.92A **10/** see tutor
- 2A) **1/** 10A **2/** 137.5v, 13.75v, 57.75v, 209v **3/** 1.75A, 5.25v
4/ 2.75A, 101.75v, 68.75v **5/** 215v, 62.5v, 40v, 112.5v
- 2AX) **1/** 10A **2/** 36v, 30v, 24v, 90v **3/** 0.33A, 8.25v
4/ 1.25A, 46.25v, 31.25 **5/** 860v, 250v, 160v, 450v
- 2B) **1/** 300v **2/** 205v, 2A **3/** 0.18A, 0.91A **4/** 1.67A, 25v each R
- 3A) **1/** 8 Ω **2/** 1.5 Ω , 1 Ω , 128v **3/** 4 Ω , 40v, 45v **4/** 30v, 115v, 23 Ω
5/ 4.5 Ω , 2.5 Ω , 5v
- 5A) **1/** 8.33A **2/** 10A, 3.64A, 1.36A, 5A **3/** 16.43A, 2.53A, 2.95A, 10.95A
4/ 15A, 9A, 3.75A, 2.25A **5/** 2.5A, 0.71A, 1.79A
- 6A) **1/** 467A, 56v **2/** 8A, 8A, 8A, 176v **3/** 15.5A, 2.53A, 2.95A, 23 Ω
4/ 1.4A, 0.58A, 0.35A, 2.33A, 3 Ω **5/** 0.4A, 0.9A, 18v
- 7A) **1/** 1.48 Ω , 24 Ω , 12 Ω , 8 Ω , 1.48 Ω , 4.8A, 2.4A, 3A, 16.2A
- 7B) **1/** 3v, 3 Ω , 0.5A, 1.5A
- 8A) **1/** 35 Ω , 250v, 7.143A **2/** 2.56A, 10.22A **3/** 18.46A, 11.54A, 9.23v
4/ 0.56 Ω **5/** 6.17m, 3 parallel 1m lengths
6/ series – doubles, reduces, halves, reduces, reduces
Parallel – doubles, increases, halves, increases, remains the same
- 9A) **1/** 0.57v, 11.43v **2/** 2 Ω **3/** 12v

- 10A) 1/ 46Ω 2/ 279Ω 3/ 230Ω 4/ 175Ω 5/ 45Ω 6/ 136Ω
- 10B) 1/ 2.5Ω 2/ 5Ω 3/ 2.5Ω 4/ 2Ω 5/ 20Ω 6/ 15Ω 7/ 44Ω
8/ 13Ω 9/ 33.33Ω
- 10C) 1/ 92Ω 2/ 139.5Ω 3/ 60Ω 4/ 79.5Ω 5/ 123.5Ω 6/ 83.5Ω
- 10D) 1/ 70Ω 2/ 55Ω 3/ 41Ω 4/ 33.4Ω 5/ 90Ω
- 11A) 1/ 47.9Ω 2/ 45.95Ω 3/ 12.17Ω
- 11B) 1/ 47.42Ω 2/ 70.37Ω 3/ 23.76Ω
- 12A) 1/ 25Ω 2/ 24Ω 3/ 64.6Ω 4/ 8.64Ω
- 12B) 1/ 31.5Ω 2/ 48.8Ω 3/ 5.3Ω
- 15A) 1/ $3.75A$ 2/ $2A$ 3/ $290v$ 4/ $7.28A, 1.82A, 3.033A$ 5/ 7.5Ω
- 15B) 1/ $6.67A, 5.55A$ 2/ $0.723A, 0.8A$ 3/ $494.18v, 4.36A$
4/ $14.4A, 3.6A, 6A$ 5/ $17.33\Omega, 1.33A$
- 16A) 1/ $15A, 705v$ 2/ $105v, 4.2A, 1.67A, 16.66\Omega$ 3/ $1.67\Omega, 2.22\Omega, 45\Omega$
4/ $0.5\Omega, 42\Omega, 5\Omega, 5A$ 5/ $71\Omega, 14\Omega, 5.71\Omega$
- 16B) 1/ $64v, 2A, 32V$ 2/ $102v, 0.9A, 90V$ 3/ $75.88v, 1.8A, 5.5\Omega$
4/ $127V, 3.5A, 27v, 37.5\Omega, 7.71\Omega$
- 16C) 1/ $200v, 10A$ 2/ $1A, 96\Omega, 24\Omega$ 3/ 9.9Ω 4/ $386v, 45.41\Omega, 6\Omega$
- 16D) 1/ $15v, 20v, 25v, 5v, 60v$ 2/ $100v, 25v$
3/ $118.2v, 89.4v, 36.53v, 15.89v, 33.53v$
- 16E) 1/ $25v, 50v, 2.5A, 75v$ 2/ $6850v$ 3/ $262.54v, 129.16v$

Congratulations, you should now be able to complete the assessment overleaf after showing this to your tutor

assignment name.....

- 1) Write the 4 equations you would generally employ when solving calculations with **series resistors only** in the circuit.

.....

.....

.....

.....


- 2) Write the 4 equations you would generally employ when solving calculations with **parallel resistors only** in the circuit.

.....

.....


.....

.....

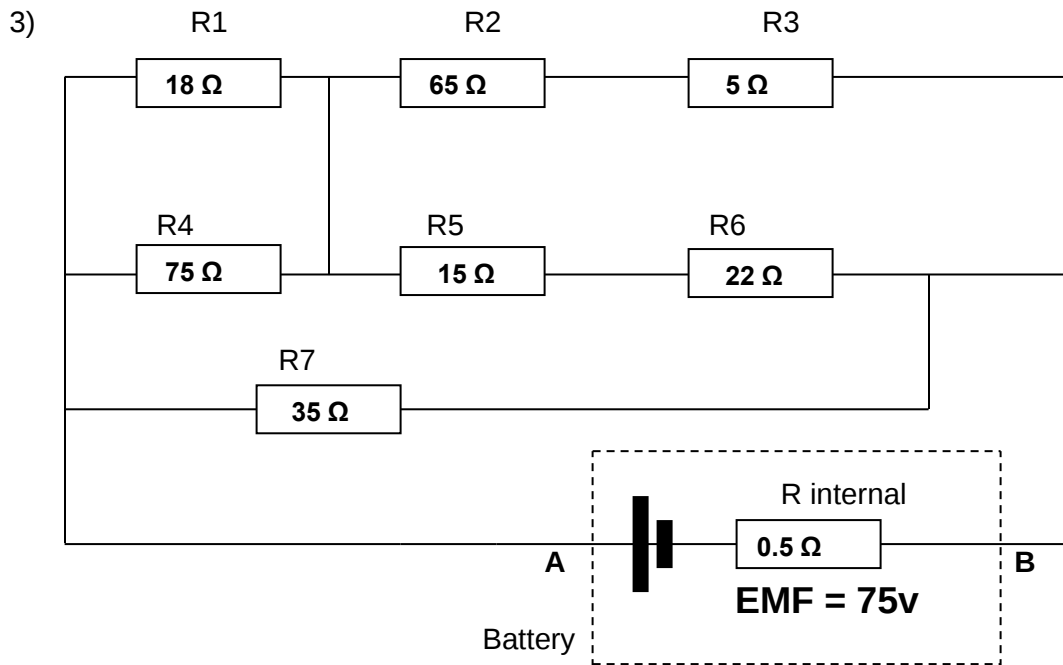



- Calculate total resistance of the external load.
- Calculate the total current.
- Calculate the voltage at the battery terminals
- Calculate the current through R_1 , R_3 , R_4 , R_5 , and R_7 .
- Calculate the voltage across R_4 , R_6

4)

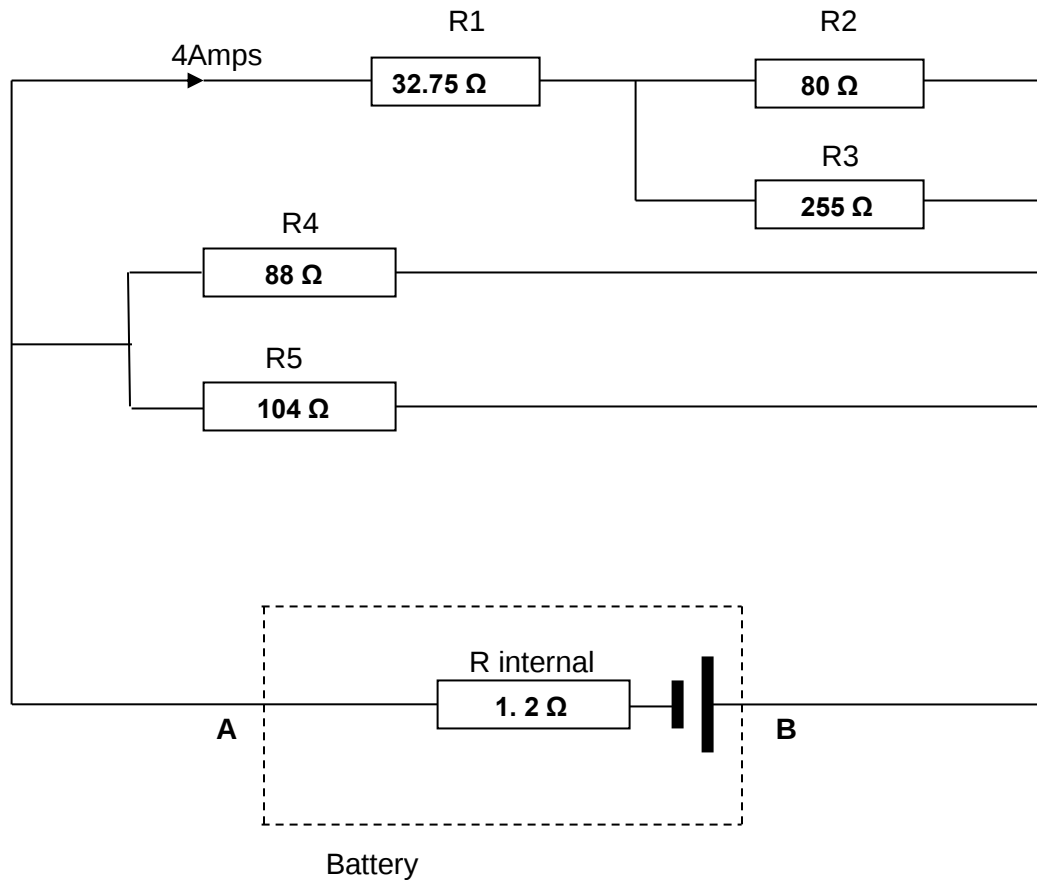

From the circuit above.

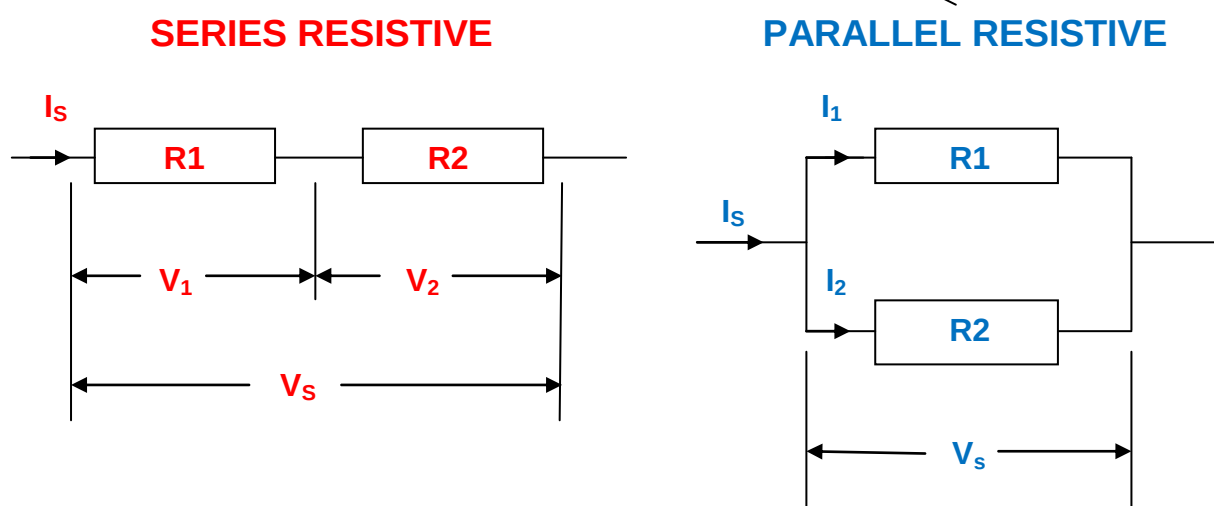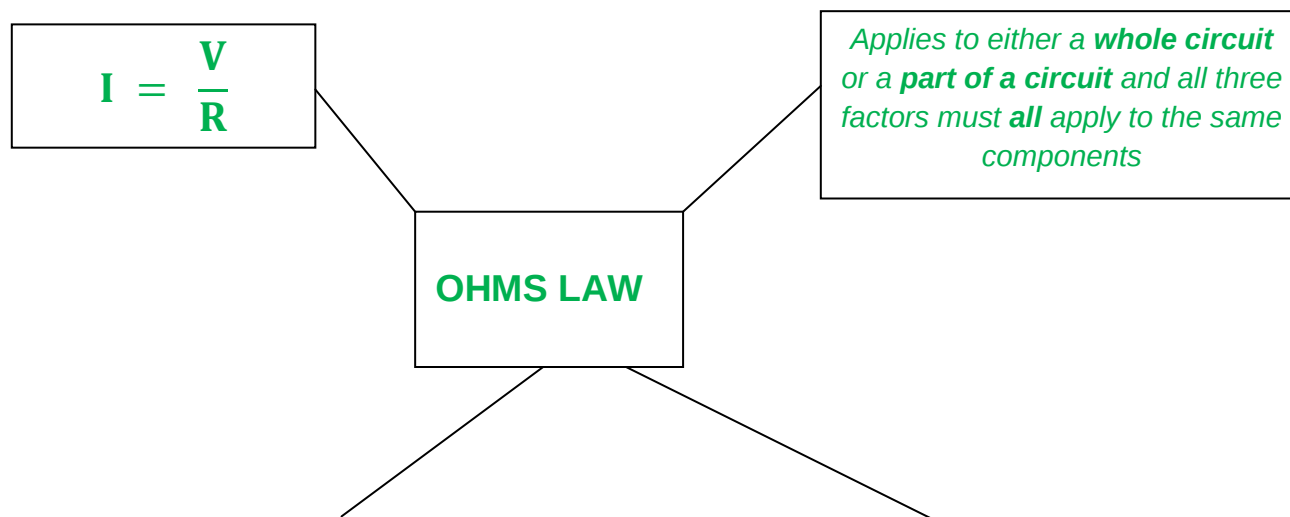- A) Calculate the total current.
- B) What is the voltage drop across R_3 .
- C) What is the value of the battery EMF



CURRENT CONSTANT		$I_s = I_1 + I_2$ <i>Kirchhoffs current law</i>
$V_s = V_1 + V_2$ <i>Kirchhoffs voltage law</i>		VOLTAGE CONSTANT
$R_T = R_1 + R_2$		$R_T^{-1} = R_1^{-1} + R_2^{-1}$