



DC fundamentals EE3103
Student workbook 2019
Power and energy theory
and calculation exercises



Student name

25070 power formulae worksheet 2

Write the three power formula below

P = Power

P =

P =

P =

Question 1



The colour bands on this resistor indicate that it has a nominal value of 1000 ohms

The physical size indicates that it has a power rating of 2 watts.

Calculate the maximum current this resistor can carry without risking it burning out

Answer question 1 (show full working)

Question 2

The resistor pictured below is rated at 500 watts and has a nominal value of 150 ohms. Calculate the power being dissipated by the resistor when 175 volts is applied across it.


Answer question 2 (show full working)



- 1) 44.7mA 2) 204 watts 3) 1323w 2645w 5290w 4) 1408 watts

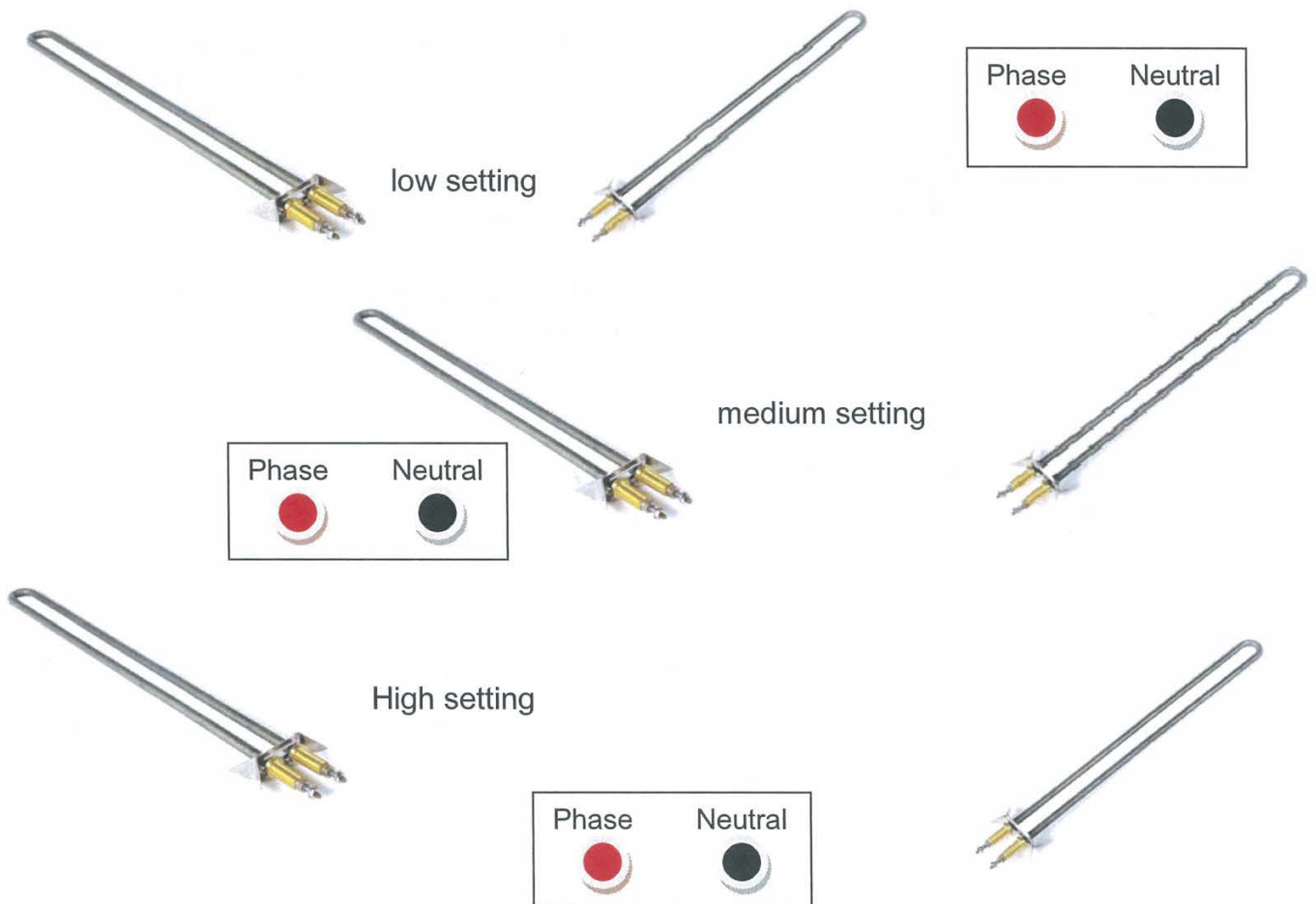Question 3

2 heater elements can be wired to achieve 3 different power settings. Low, medium or high. **Task** Wire each set of elements to achieve these three settings



Next calculate the power dissipated in each of these three settings. Each element measures 20 ohms

Answer question 3 (show full working)

Power low


Power medium

Power high

1) 44.7mA 2) 204 watts 3) 1323w 2645w 5290w 4) 1408 watts

Question 4

These 6 resistors are all 10 ohms each

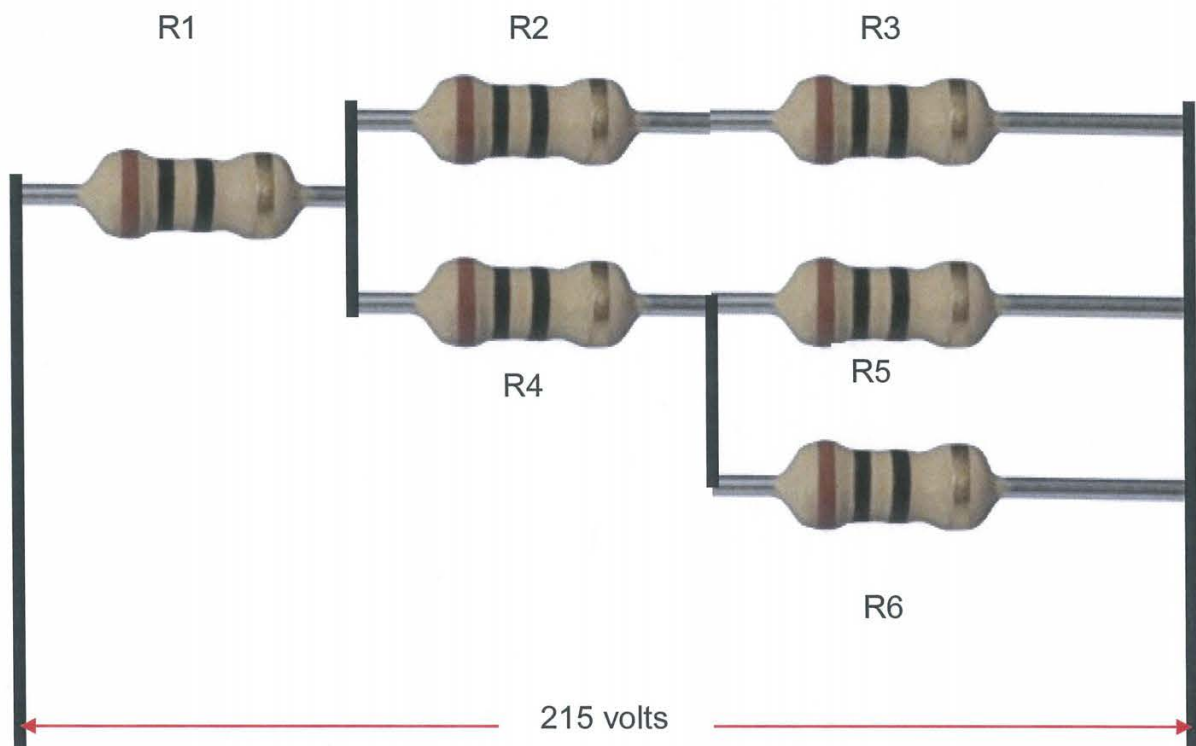

Calculate the power dissipated by each resistor and the total power dissipated by the complete circuit (show all working)

Answers

Power R1 =

Power R2 =

Power R3 =

Power R4 =

Power R5 =


Power R6 =

Power total =

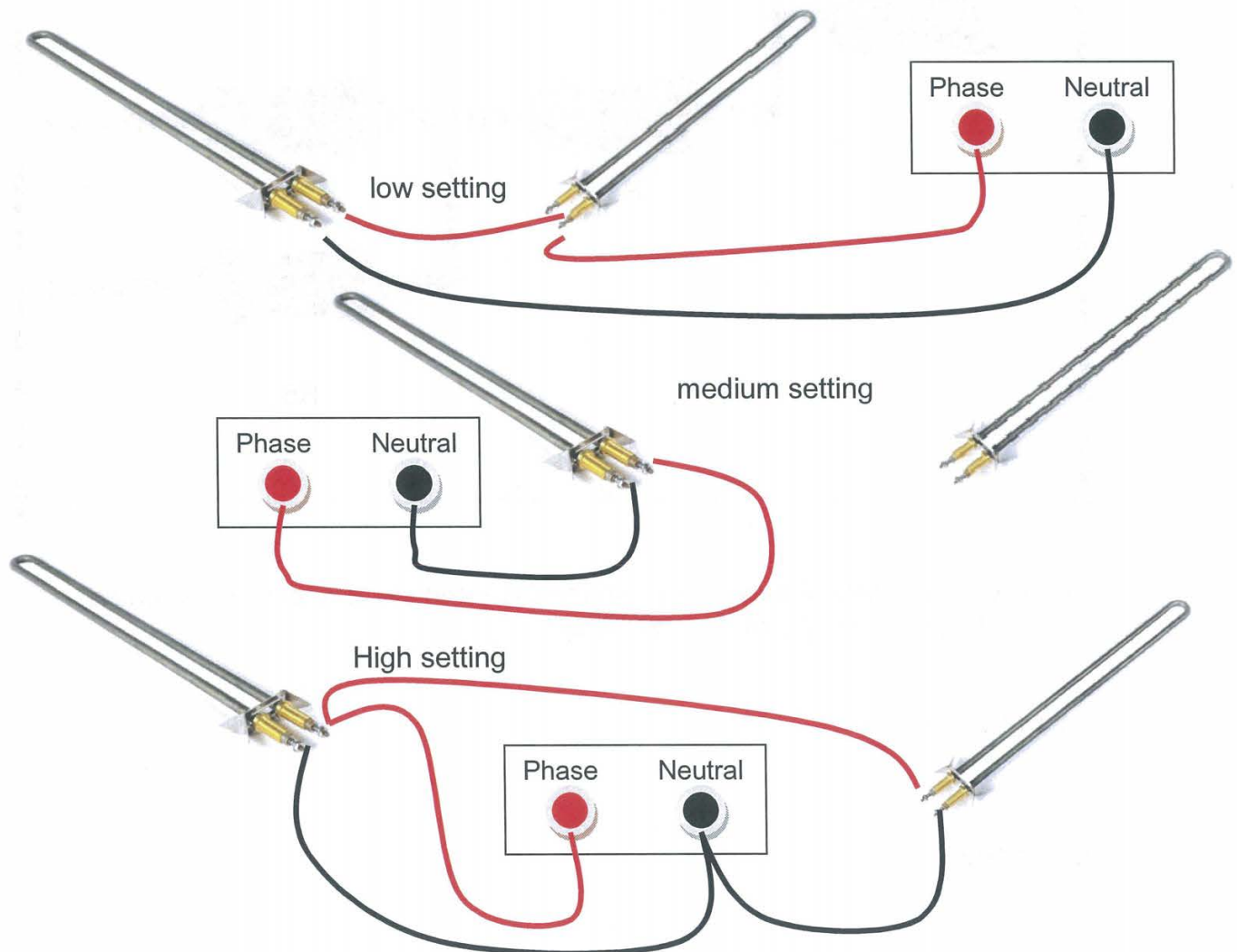1) 44.7mA 2) 204 watts 3) 1323w 2645w 5290w 4) 1408 watts

25070 power formulae worksheet 2 **ANSWERS** Question 3

2 heater elements can be wired to achieve 3 different power settings. Low, medium or high. **Task** Wire each set of elements to achieve these three settings



Next calculate the power dissipated in each of these three settings.
Each element measures 20 ohms

Answer question 3 (show full working)

Power low


Power medium

Power high

1) 44.7mA 2) 204 watts 3) 1323w 2645w 5290w

Question 4

These 6 resistors are all 10 ohms each

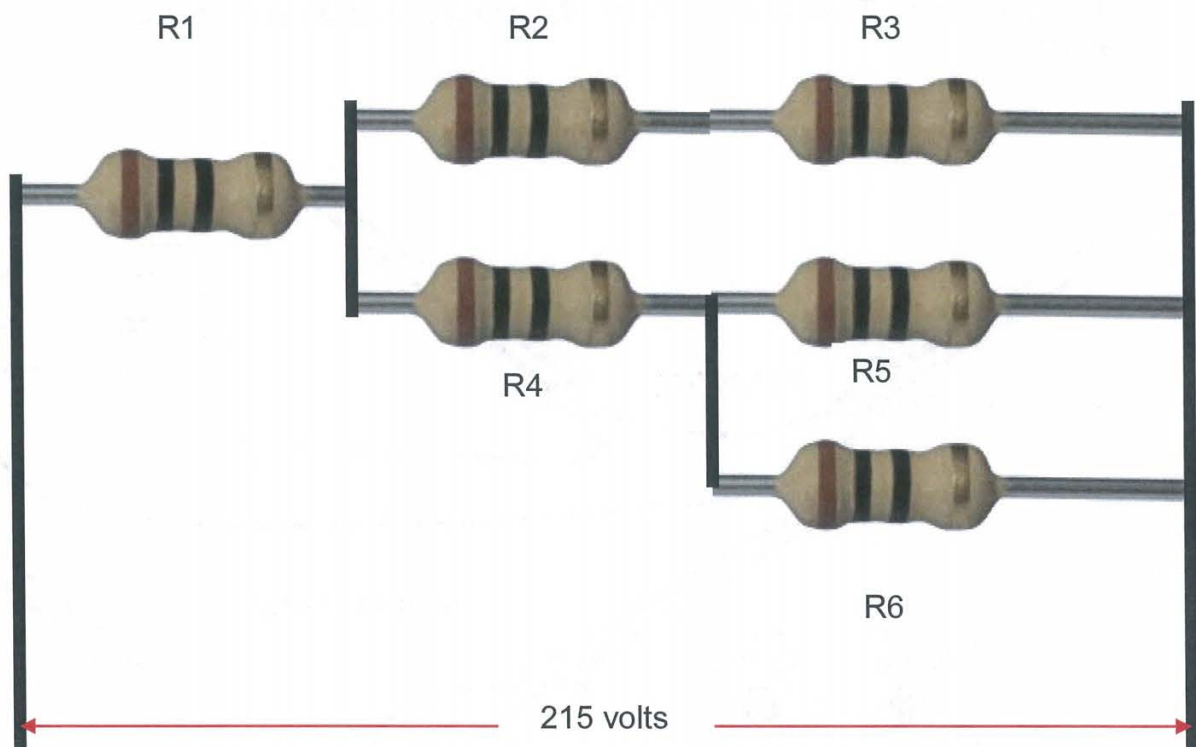

Calculate the power dissipated by each resistor and the total power dissipated by the complete circuit (show all working)

$$R_t = (20 // 15) + 10$$

$$R_t = 18.57\Omega$$

$$I_s = \frac{215V}{18.57\Omega}$$

$$I_s = 11.58A$$

$$\text{Power } R1 = 11.58^2 \times 10 = 1341w$$

$$V_D \text{ } R1 = 11.58 \times 10 = 115.8V$$

Therefore 49.6 v across R2 and R3 each

$$\text{Power } R2 = 246w$$

$$\text{Power } R3 = 246w$$

$$\text{Current through } R4 = \frac{99.2V}{15\Omega} = 6.61A$$

1) 44.7mA 2) 204 watts 3) 1323w 2645w 5290w

$$\text{Power R4} = 6.61^2 \times 10 = 437\text{w}$$

And as current in R5 and R6 is half input current

$$\text{Power R5} = 3.305^2 \times 10 = 109\text{w}$$

$$\text{Power R6} = 109\text{W}$$

$$\text{Total power} = 109 + 109 + 437 + 246 + 246 + 1341 = 2488 \text{ watts}$$

$$\text{Total power} = 11.58^2 \times 18.57 = 2490 \text{ watts}$$

$$\text{Power R1} = 1341\text{w}$$

$$\text{Power R2} = 246\text{w}$$

$$\text{Power R3} = 246\text{w}$$

$$\text{Power R4} = 437\text{w}$$

$$\text{Power R5} = 109\text{w}$$

$$\text{Power R6} = 109\text{w}$$

$$\text{Power total} = 2490\text{w}$$