



DC fundamentals EE3103
Student workbook 2019
Power and energy theory
and calculation exercises



Student name

25070 Power and energy and the cost to run worksheet 5

Write the three power formula below


P = Power

P =

P =

P =

Question 1

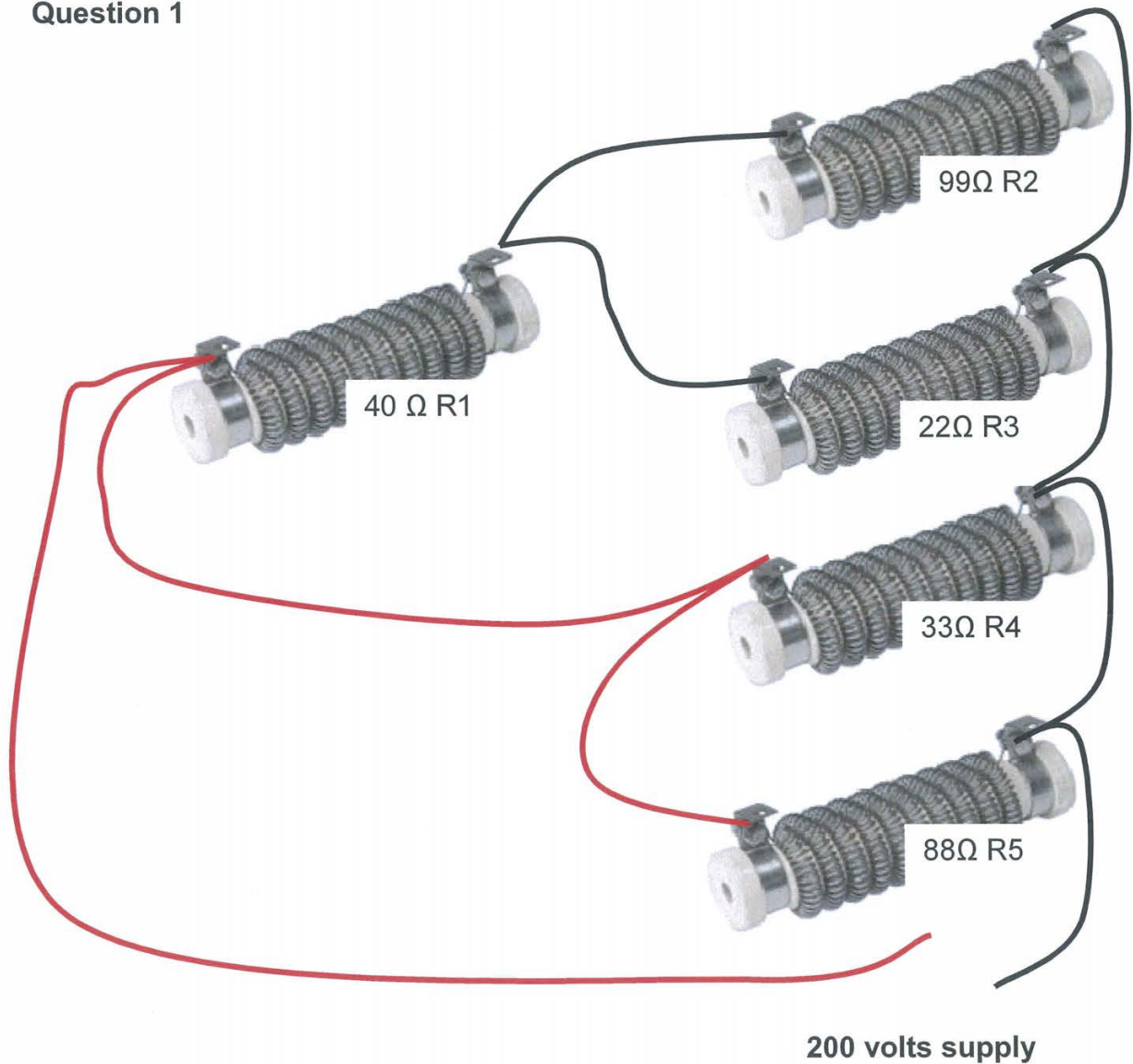

- Calculate from the circuit drawn above what the power dissipation is for the total circuit
- Calculate the power dissipated in each individual resistor
- Calculate the cost to run the whole circuit for 10 hours with a tariff of 27 cents per unit

1) a) 2356W b) R1 469W R2 39W R3 175W R4 1212W R5 454W c) \$6.34
2) a) 203.94V b) 366W c) \$27.38

Blank page for working question 1 worksheet 5

1) a) 2356W b) R1 469W R2 39W R3 175W R4 1212W R5 454W c) \$6.34
2) a) 203.94V b) 366W c) \$27.38

Question 2

A 230 volt TPS cable supplies a heater that has a 15 ohm element.

The TPS cable has 0.5 ohms resistance in the phase conductor and has 0.5 ohms resistance in the neutral conductor.

The cable was damaged during installation and was joined in a connection box in the neutral wire. The terminal wasn't tightened sufficiently at this join and resulted in an extra cable resistance of 1 ohm.

Draw a circuit diagram of the above information and use that to calculate the following

- a) The voltage across the heater element
- b) The power dissipated in the cable (including the repair joint)
- c) The cost to run the heater for 40 hours (including the power dissipated in the cables) at a tariff of 22 cents kWh