



WeiTec

Te Whare Wānanga o te Awakairangi

A

DC fundamentals EE3103

Student workbook 2020 for Ohms and Kirchhoffs laws with Series and parallel exercises




Student name


SERIES CIRCUIT CALCULATIONS
WORKSHEETS 2A, 2B, 3A

Ohms Law. **Work Sheet 2A** **Series calculations.**


Fill out this triangle now

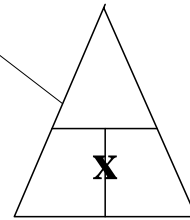

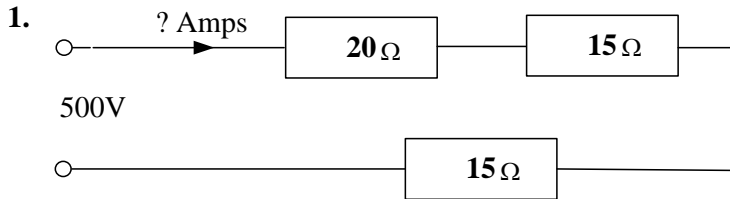
Determine the unknown value(s).
 Layout your workings on another page.




Answer = Amps

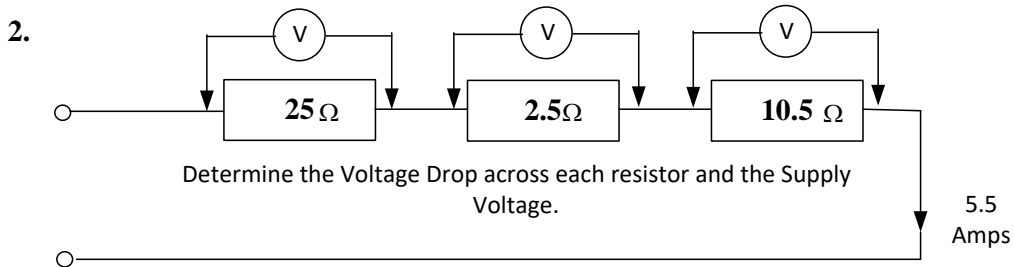

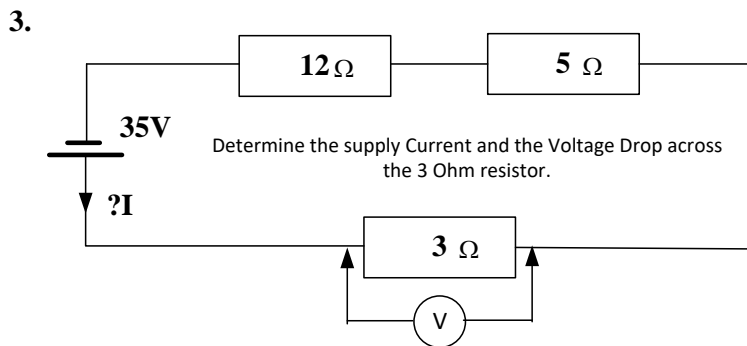
Answers: $V_{25} =$ $V_{2.5} =$ $V_{10.5} =$
 $V_s =$



Answers: $I_s =$ $VD_3 =$

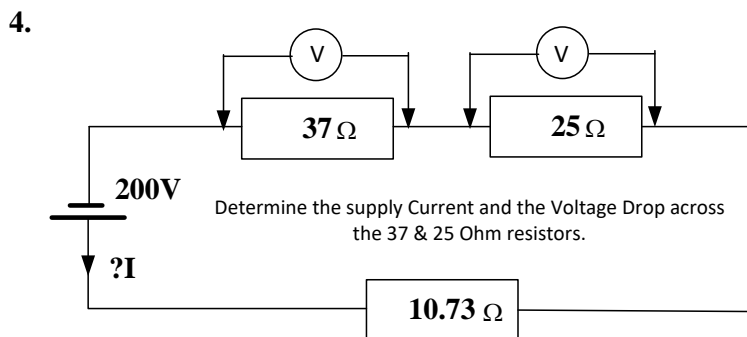


Answers: $I_s =$ $VD_{37} =$ $VD_{25} =$

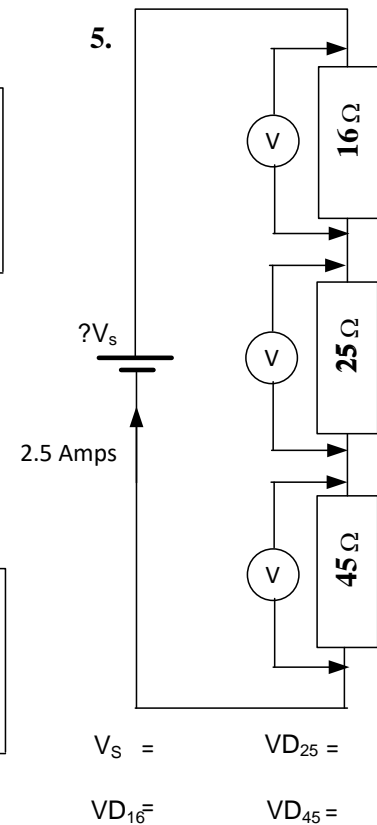


Ohms Law. Work Sheet 2B Series calculations.


Fill out this triangle now

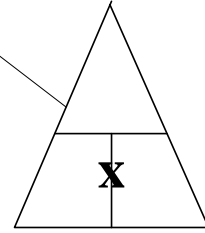

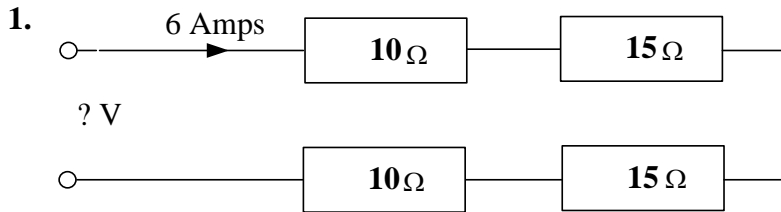
Determine the unknown value(s).
Layout your workings on another page.



Answer = Volts

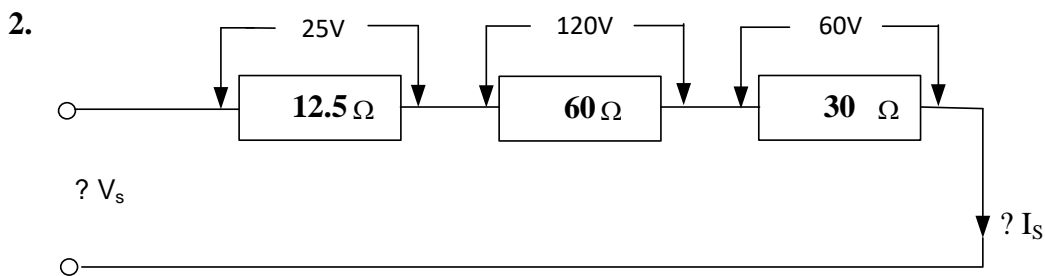

Answers: $V_s =$ Volts $I_s =$ Amps

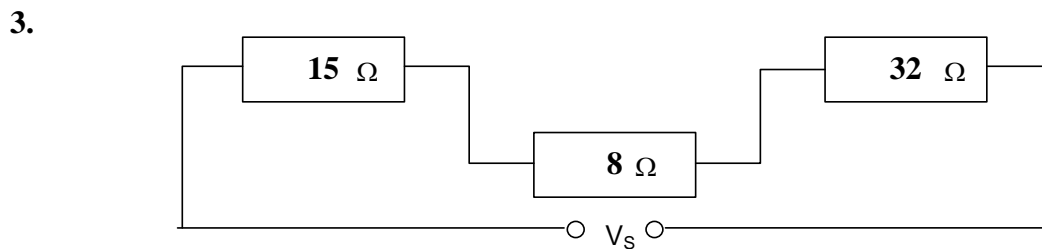

Determine the total current flow if
the Supply Voltage (V_s) is:

a. 10 Volts
 $I =$



b. 50 Volts. $I =$

4. Four resistors are connected in series. Each resistor has a resistance of 15 Ohms. If the supply Voltage is 100 Volts, what is the current drawn from the supply and what Voltage Drop would be measured across each resistor. Draw the circuit below (neatly) and show on it your calculated answers.


Determine the ? value(s).
Layout workings on another sheet

Ohms Law. **Work Sheet 3A** **Hard Series calculations.**

Fill out this triangle now

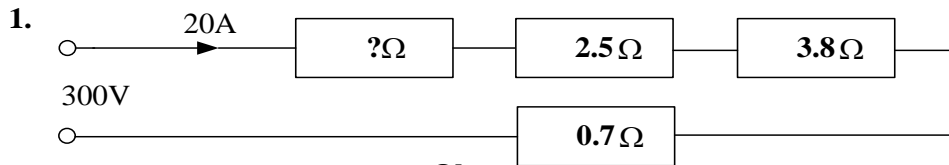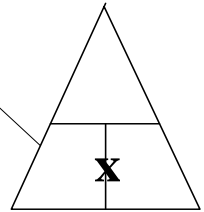


Answer: $R_7 =$ Ohms

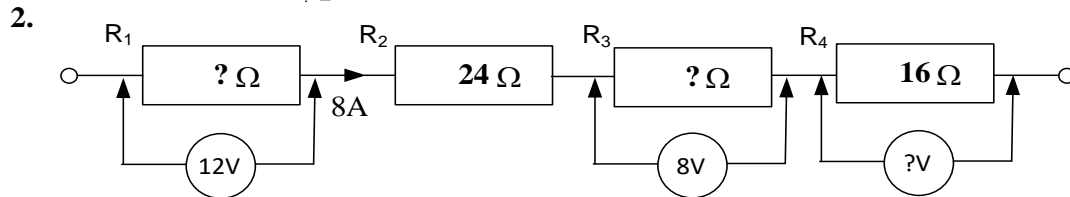


Answers: $R_1 =$ $R_3 =$ $V_{R4} =$

Supply Voltage =

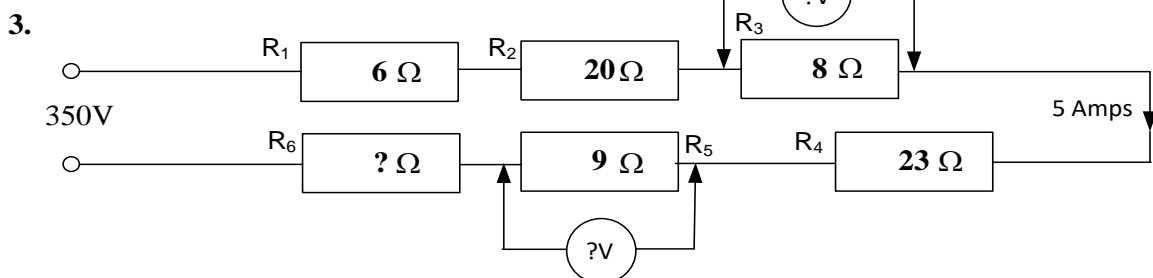


Answers: $R_6 =$ $V_{R3} =$ $V_{R5} =$

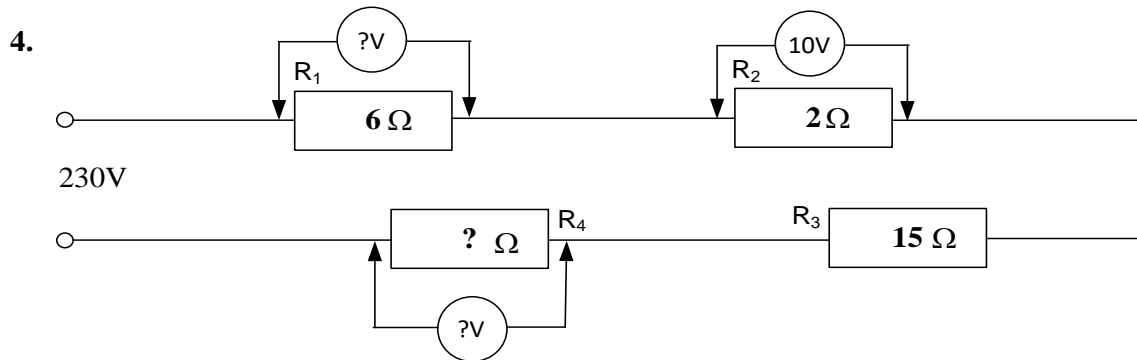

Answers: $V_{R1} =$ $V_{R4} =$ $R_4 =$

Total Current =

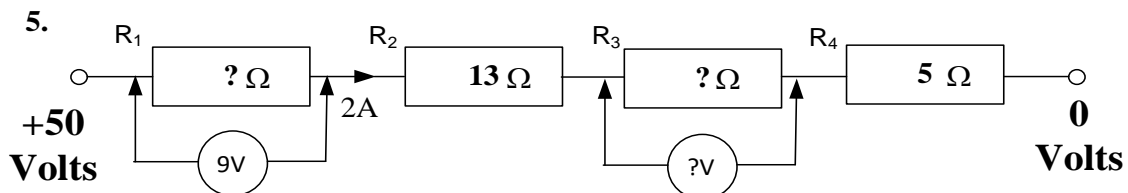

Answers: $R_1 =$ $R_3 =$ $V_{R3} =$