



WeiTec

Te Whare Wānanga o te Awakairangi

A

DC fundamentals EE3103

Student workbook 2020 for Ohms and Kirchhoffs laws with Series and parallel exercises



Student name

INTERNAL RESISTANCE


WORKSHEETS 9A, 16D, 16E

Work Sheet 9A

Internal Resistance of a power supply - e.g. Battery.


The internal resistance is represented by a series resistor within the source.

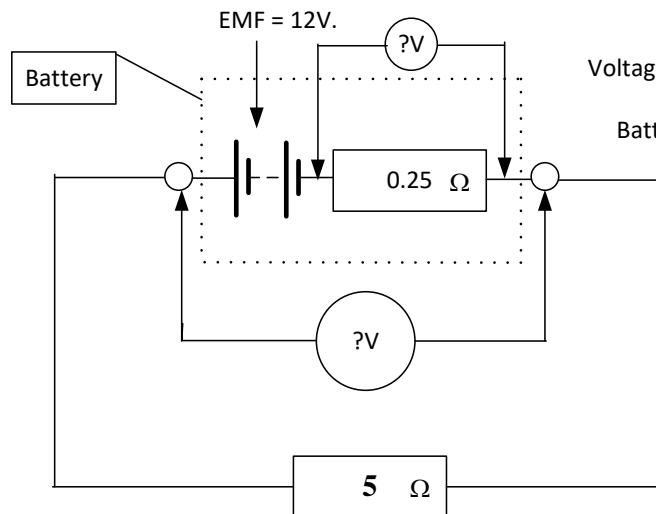1. A battery has an EMF of 12 V and an internal resistance of 0.25 Ohms.
Find the drop in voltage across the battery output terminals when a load of 5 Ohms is applied and the battery output Voltage?.



Answers:
Voltage Drop across internal resistance. = Volts.
Battery output Voltage. = Volts.

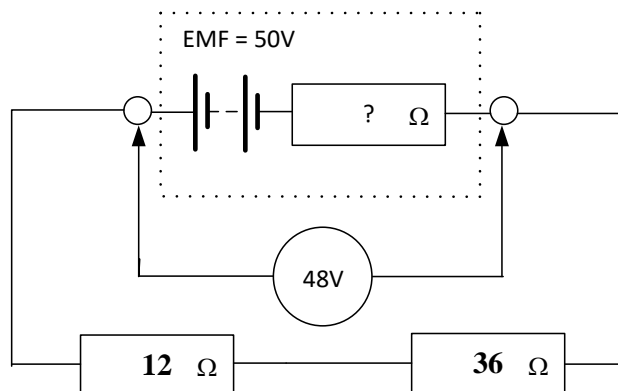2. Determine the value of the internal resistance?.




Answer = Ω

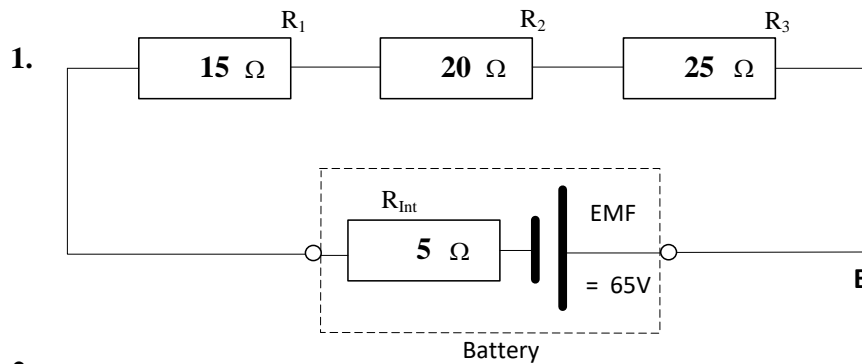3. Ten 1.5V cells are connected in series. Each cell has an internal resistance of 0.15 Ohms. What would be the Voltage across a 6 Ohm load resistor placed across the complete battery?. (Hint - Draw the circuit here)

Answer = Volts.

Ohms Law.
Work Sheet 16D
Harder Series-Parallel calculations.



Answers:

V_{R1} = Volts


V_{R2} = Volts

V_{R3} = Volts

V_{Int} = Volts

Battery output Voltage


= Volts

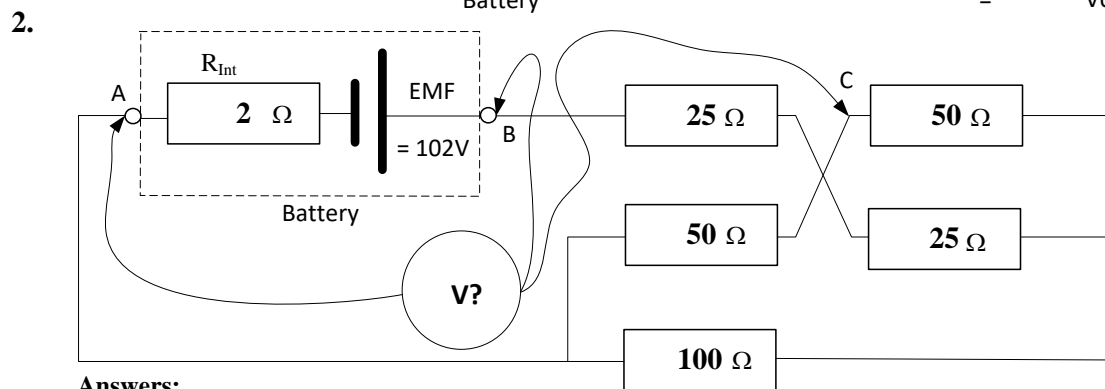

Answers:

V_{A-B} = Volts

V_{A-C} = Volts

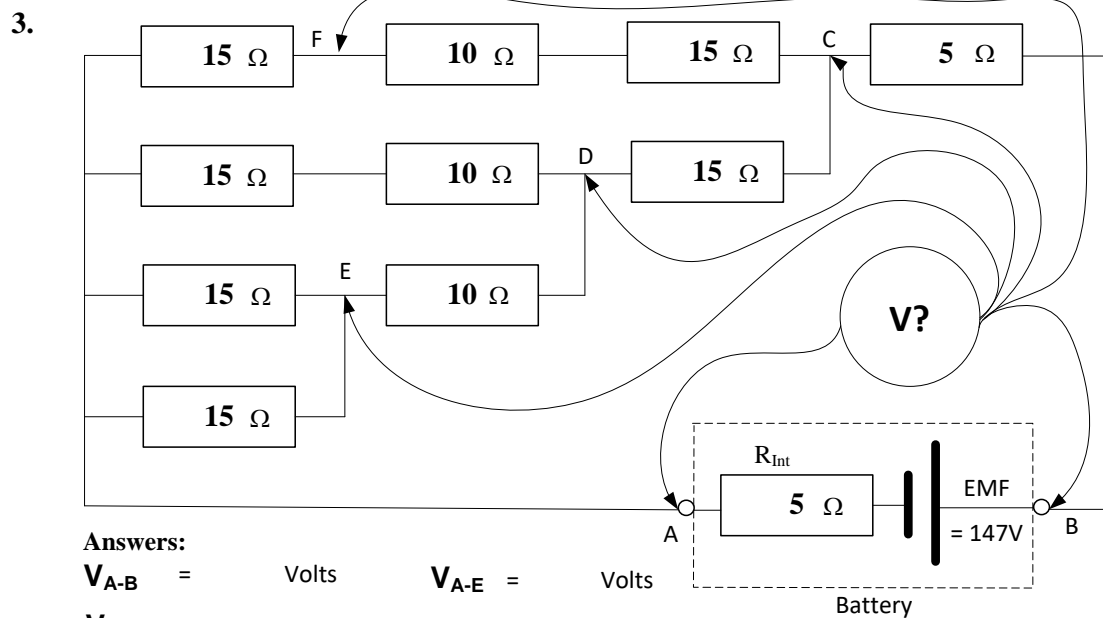

Answers:

V_{A-B} = Volts


V_{A-E} = Volts

V_{A-C} = Volts

V_{A-F} = Volts

V_{A-D} = Volts

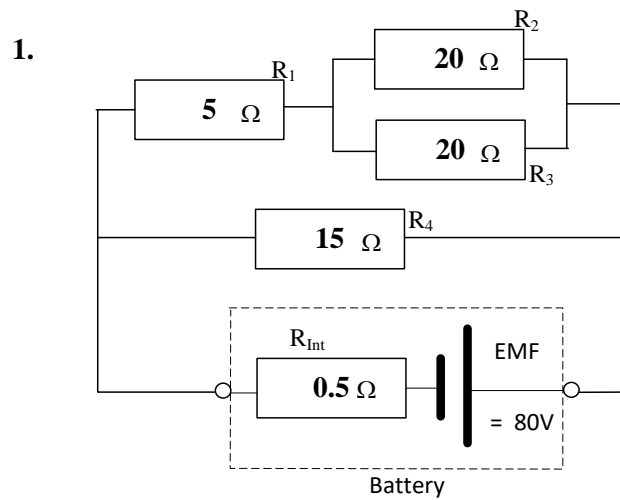Ohms Law.
Work Sheet 16E
Harder Series-Parallel calculations.



Find:

V_{R1} = Volts

V_{R2} = Volts

I_{R3} = Amps


Battery output Voltage

= Volts


2. If the current through R_2 is 7.5 Amps, find:

The EMF produced by the Battery

= Volts

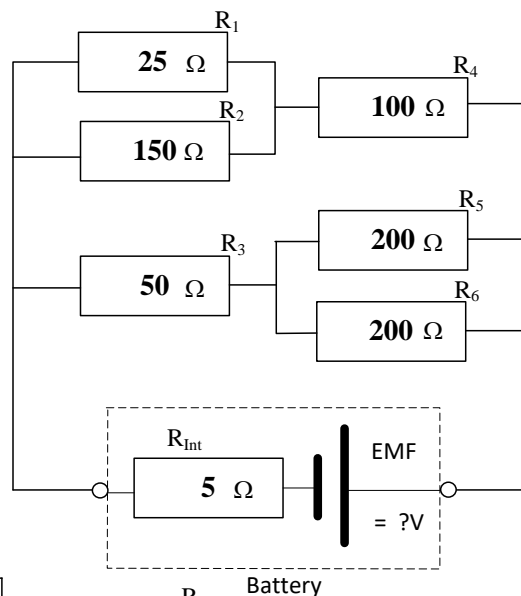

3.

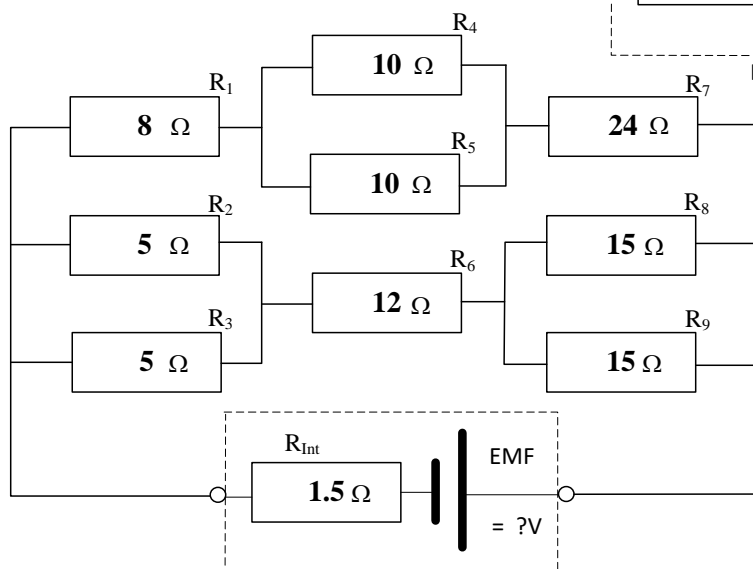

If the Voltage measured across R_5 is 32 Volts, find:

The EMF produced by the Battery

= Volts &,

The Potential Difference that would be measured across R_6

= Volts